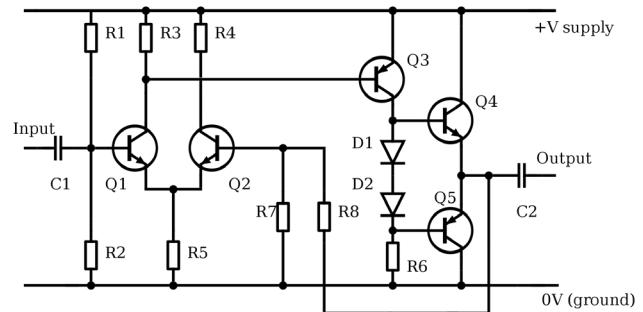


Lecture 5 – Electronics

Andrés Faíña (anfv@itu.dk)



Materials

Ask for materials to TAs or me

Use leftovers (box next to the laser cutter)

Quality of the prints

Do you really need (extra) fine quality?

Increase layer height to 0.2mm (or 0.3 if nozzle >0.6mm)

Think before cut!

Put your part next to previous cuts or edges

Do not cut your part in the centre of the sheet

Group project

Projects:

Mechanics, Electronics and Embedded Programming Works (problems should be documented)

Good technical documentation

Project mode: 1 month (plan in advance), start now

Reuse open source/DIY projects is allowed, but:

cite them

try to improve/modify them, mention the changes

Doubts about topic, scope, etc., **ask!**

Group project ideas



Overview

Basic electronics

- Power supply

- Multimeter

- Basic circuits with resistors

- Schematics

Sensors

- Basic sensors: Switch, potentiometer

Motors

- DC motor with switches

Transistors



Voltage and Current

Voltage (V): electric potential energy per unit charge
or electric potential


Current (A): flow of electric charge

Resistance (Ω): difficulty to pass an electric current
through a conductor



$$V = R * I$$

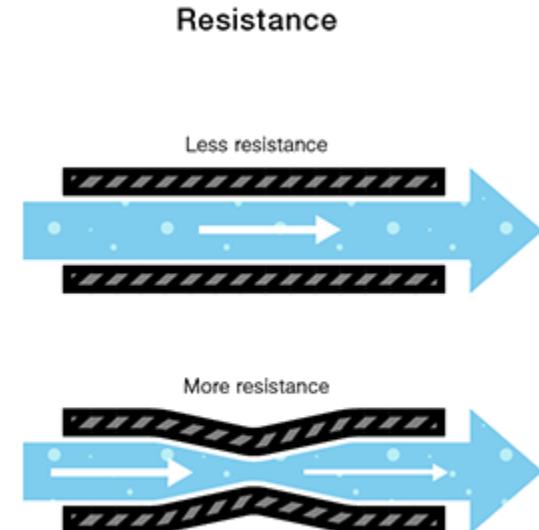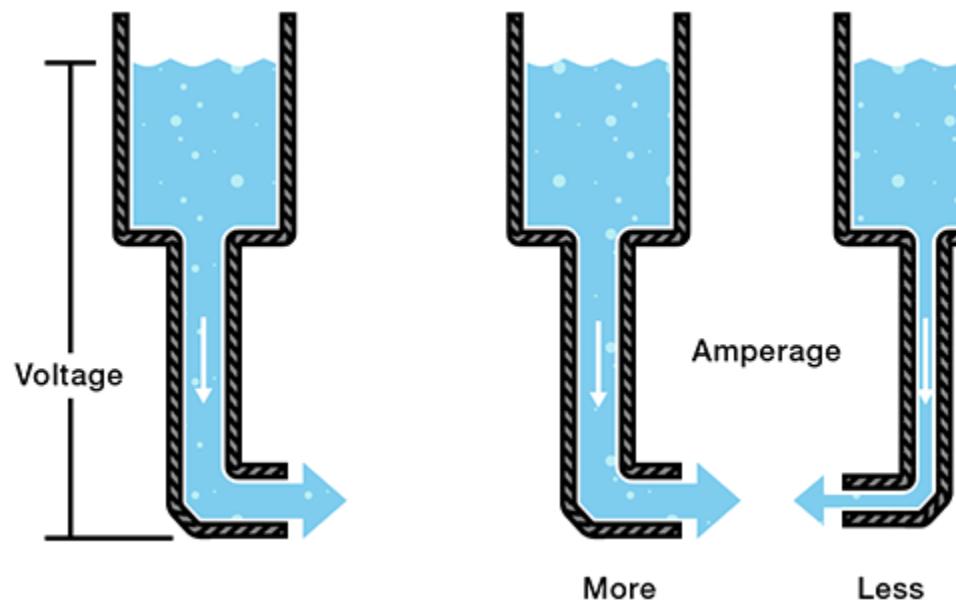

Power supply

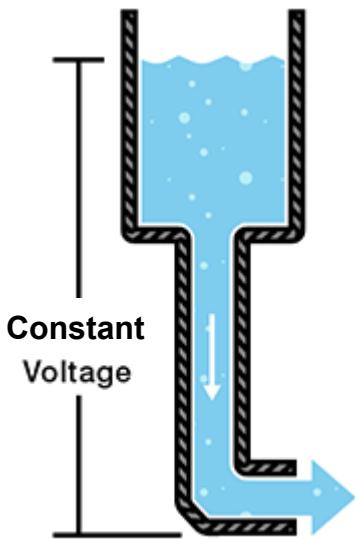

Resistors

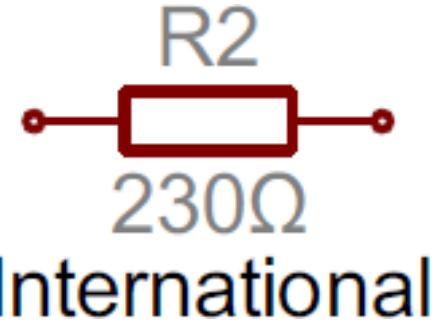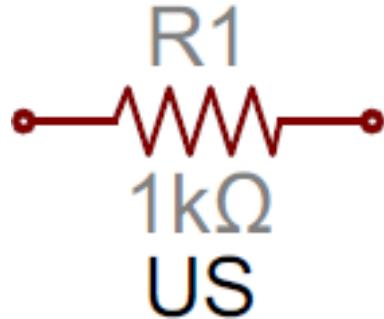


Limit the amount of current that flows through a circuit
Component with **2 terminals**
No polarity

$$V = R * I$$

Multimeter

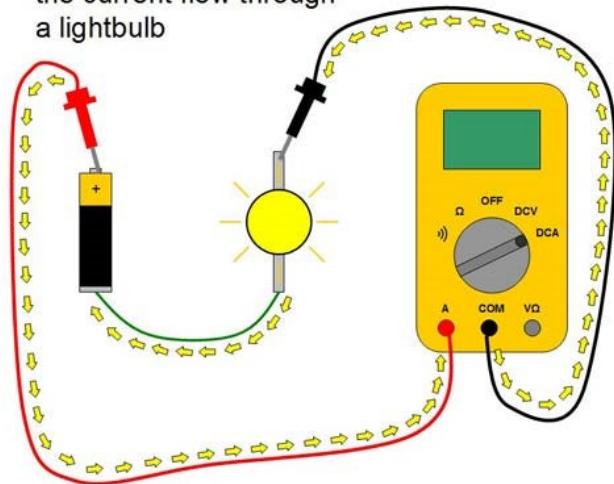Connect a multimeter in **series** to measure the current flow through a lightbulb




Current mode

High current measurements

Current mode
Low current measurements



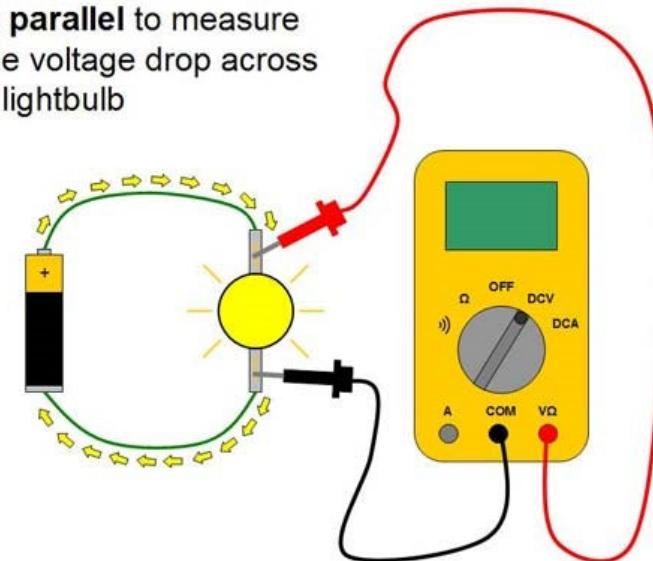Connect a multimeter in **parallel** to measure the voltage drop across a lightbulb




Mode selector

Voltage mode
Voltage, resistance
measurements

COM
(Reference)
Always connected

Setup (2 min)

Power Supply

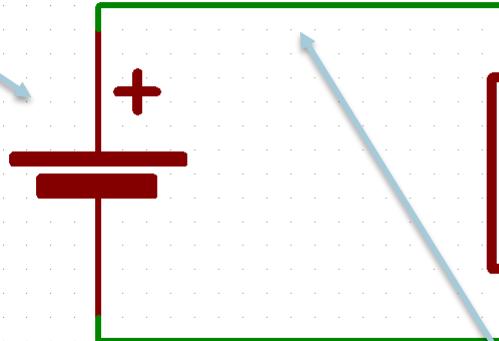

Resistor

R1
1k

Wires

Take a


Power supply (or battery holder)

A red and blue solid wire

A multimeter

An Arduino kit

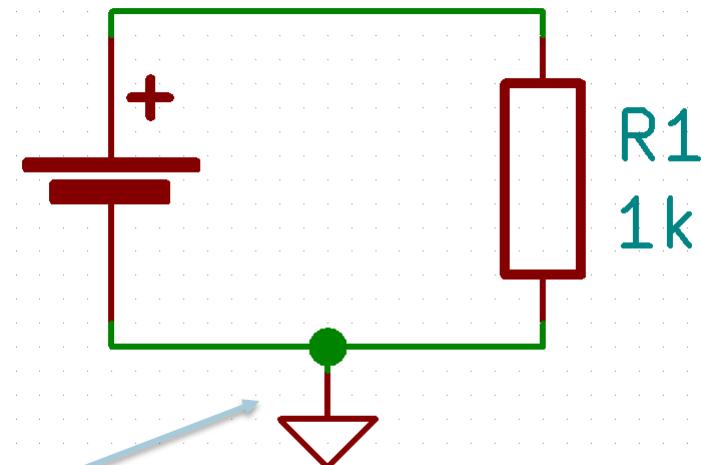Reference
(This point has 0V
by convention)



GND

Exercise #0

Test the Ohm's law

Connect a resistor to a power supply

Vary the voltage (<15V)

Check voltage and current

Measure voltage with a multimeter

Calculate resistance ($R=V/I$)

Power off the power supply and check resistance with a multimeter

How to read schematics


Electronic schematics or circuit diagrams represent an electrical circuit:

Components





Resistors, Capacitors, ICs

Connections between components

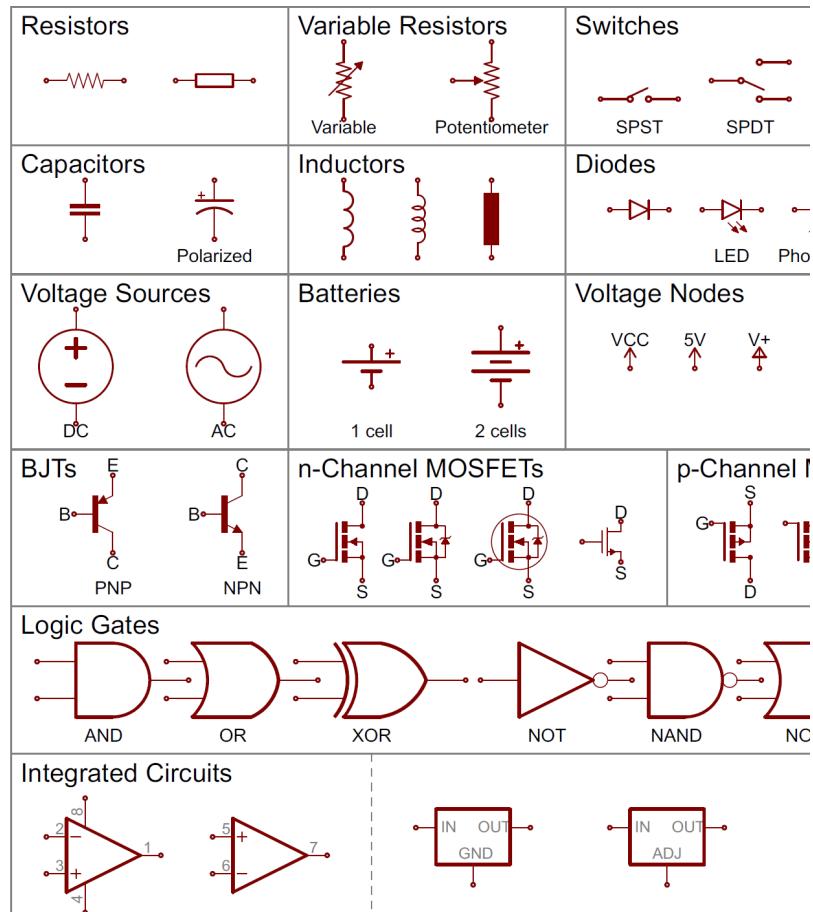
<https://learn.sparkfun.com/tutorials/how-to-read-a-schematic>




Basic components

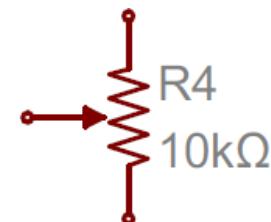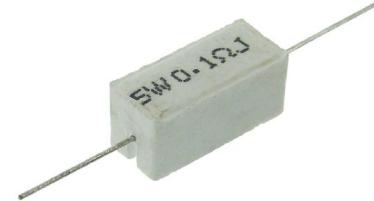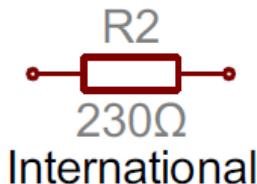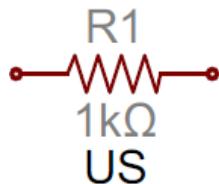



Potentiometer

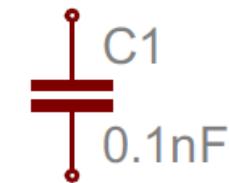


Non-polarized

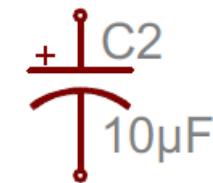


Polarized

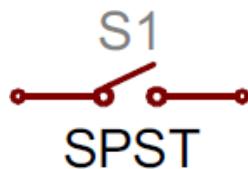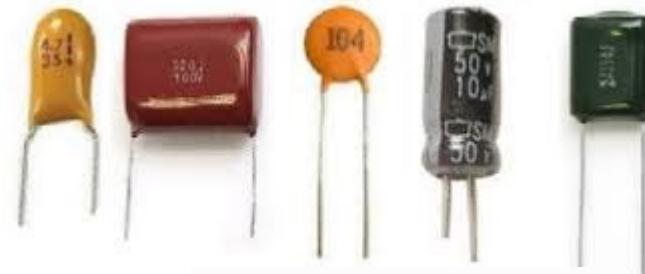

Diode

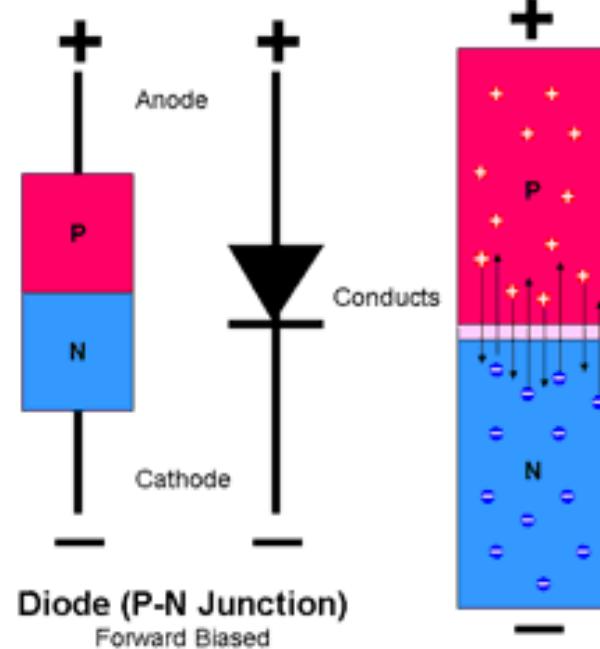

Forward biased diode

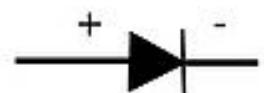

Electron flow




Current flow



Depletion layer



Reverse biased diode

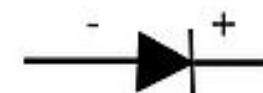

Electron flow - None

Current flow - None


Depletion layer





2 terminal
Polarity
If current flows => $V \approx 2.1v$




A LED is a
diode that
emits light!

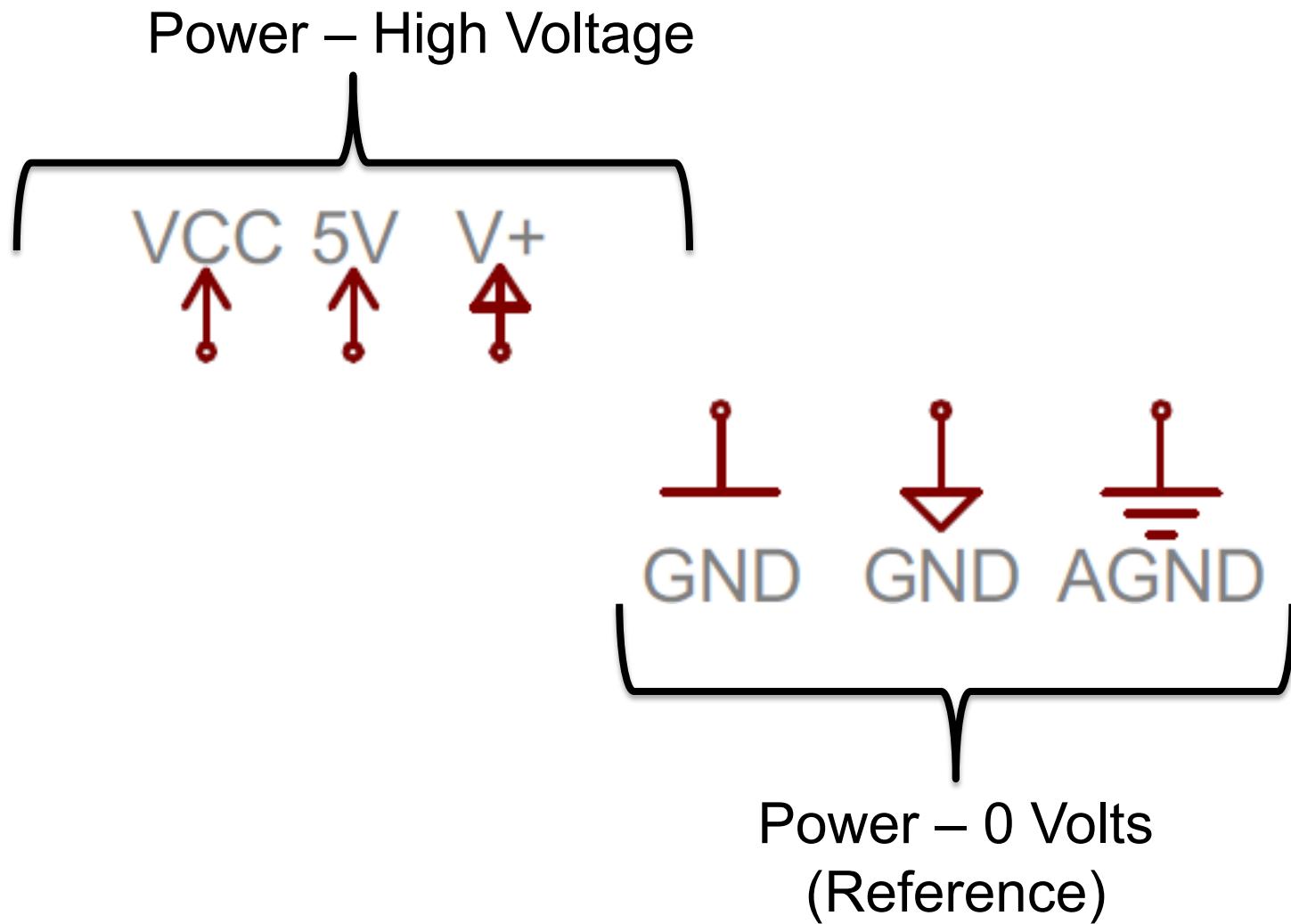

Connections – Wires and junctions

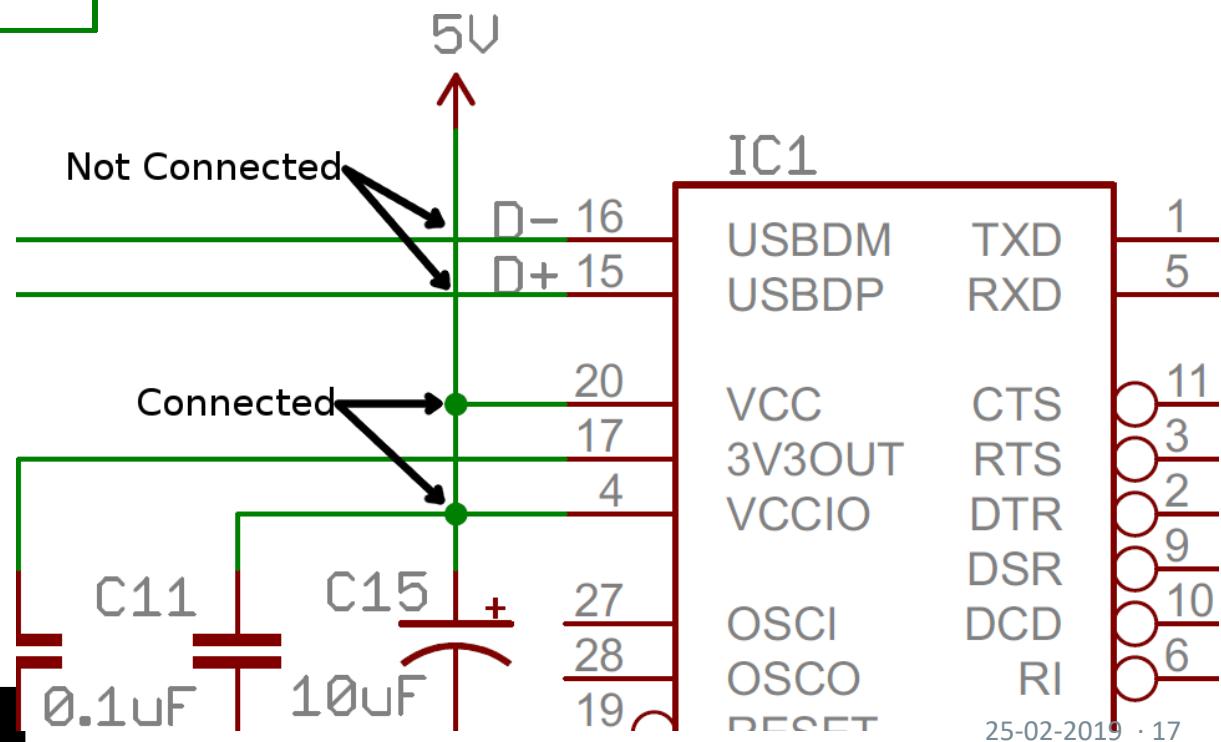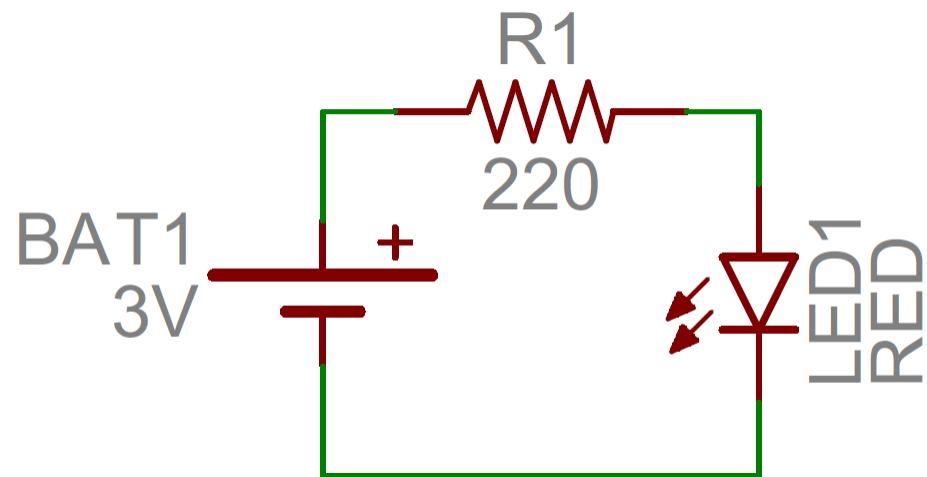

Exercise #1: Your first circuit

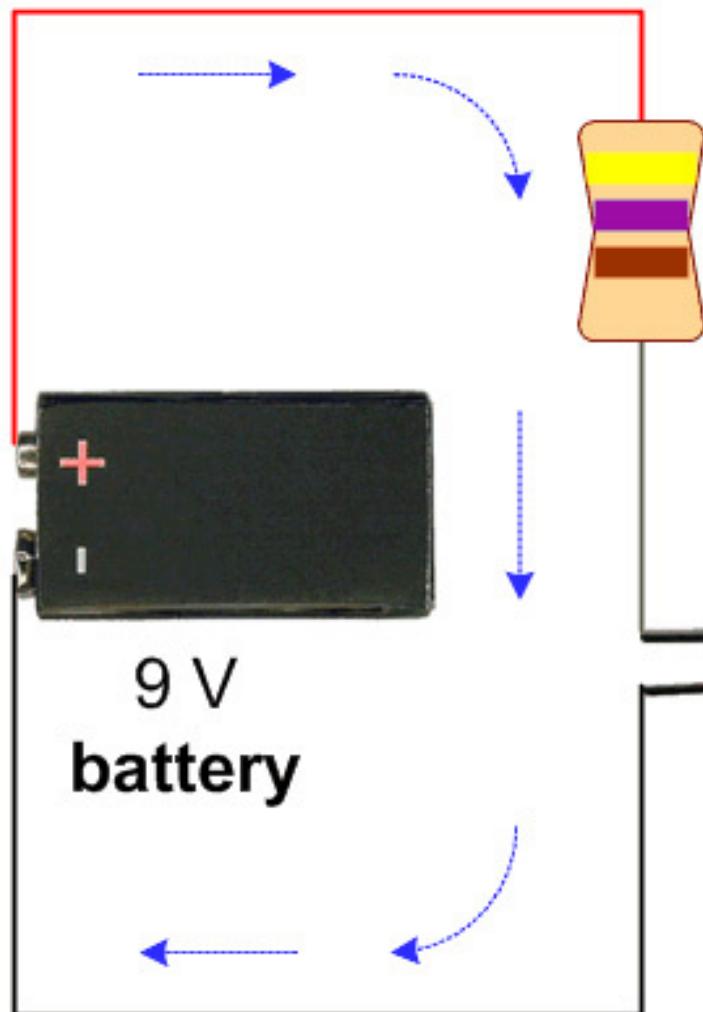

resistor
470 Ω
(yellow, violet,
brown)

or




350 Ω
Orange, Green, Brown


Breadboards

How to Use a Breadboard


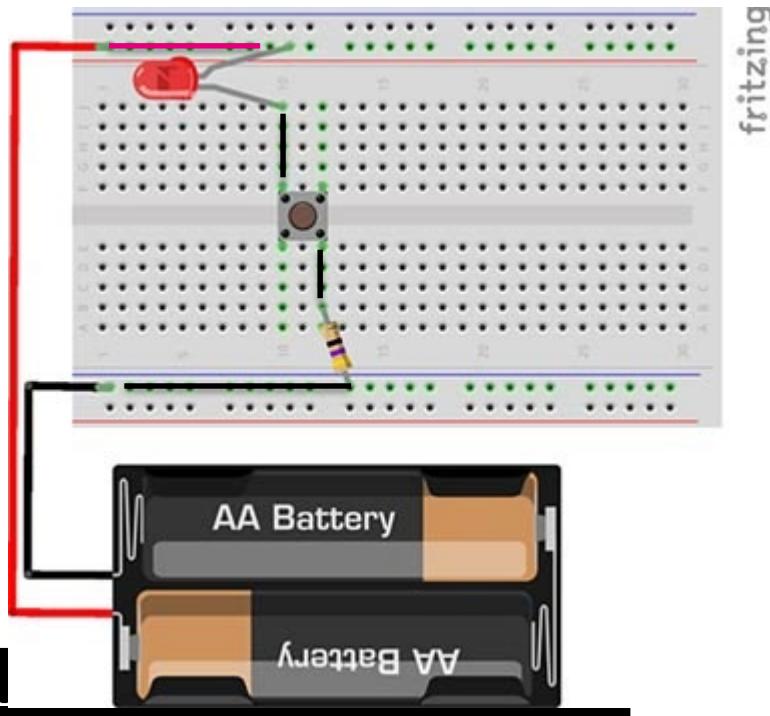
<https://learn.sparkfun.com/tutorials/how-to-use-a-breadboard>



fritzing

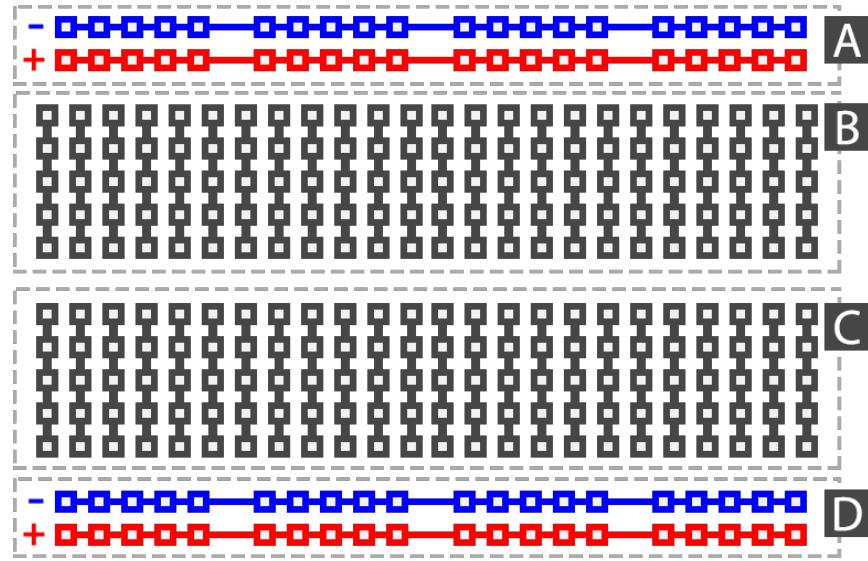


Your first circuit

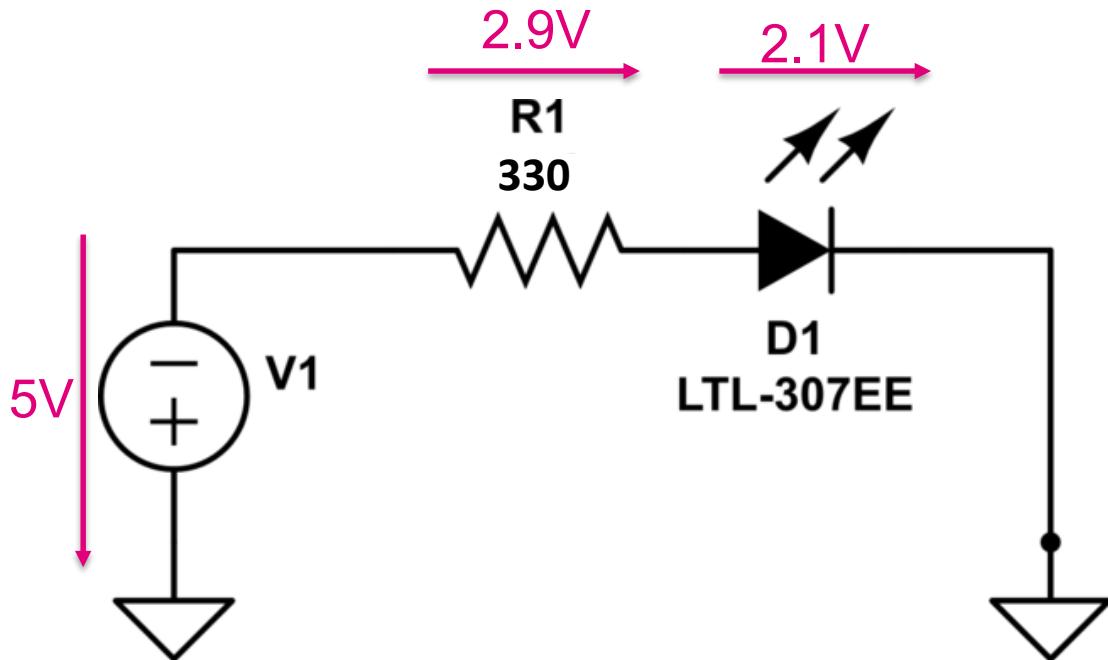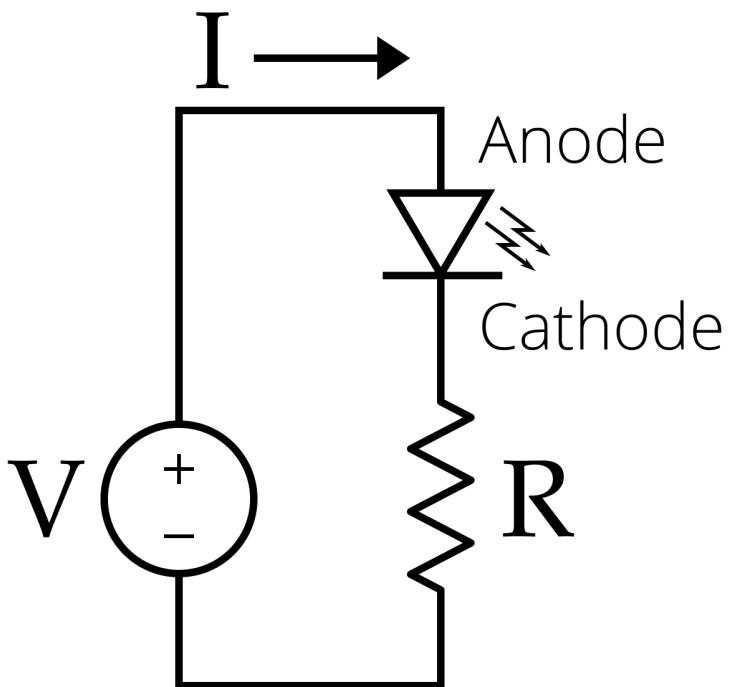


$$I = V/R = 2.9/330 = 0.009A = 9mA$$

What happens if we don't add the resistor???

Resistors in series/parallel

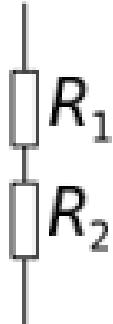


$$R_{TOTAL} = R_1 + R_2 \dots R_n$$

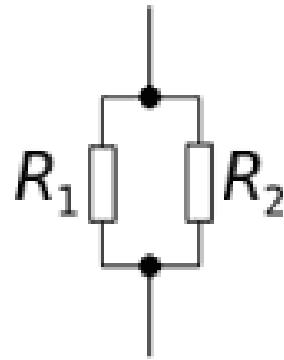

$$\frac{1}{R_{TOTAL}} = \frac{1}{R_1} + \frac{1}{R_2} \dots \frac{1}{R_n}$$

Voltage divider

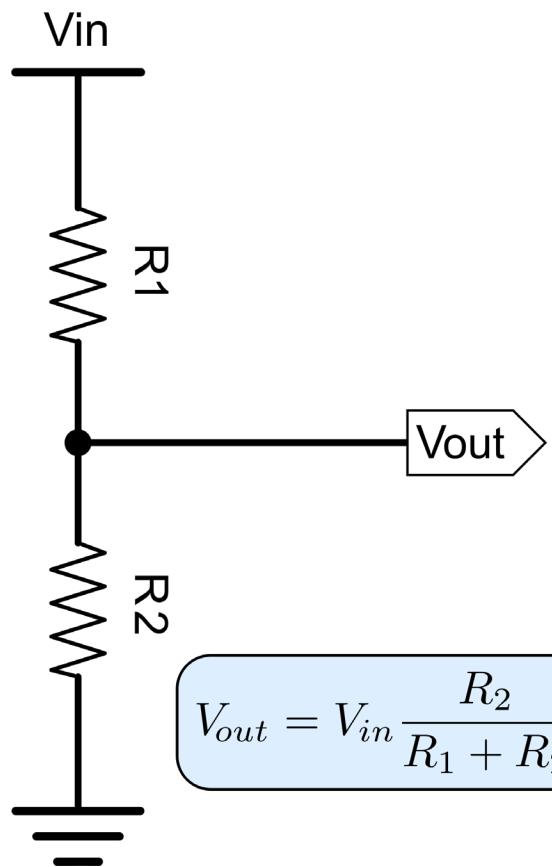

Sensing physical properties of the world

List of simple sensors


- Switches
- Resistive position sensors (Potentiometer)
- Light sensors
- Reflective optosensors
- Break beam optosensors

Switch and potentiometer



Switch







Potentiometer

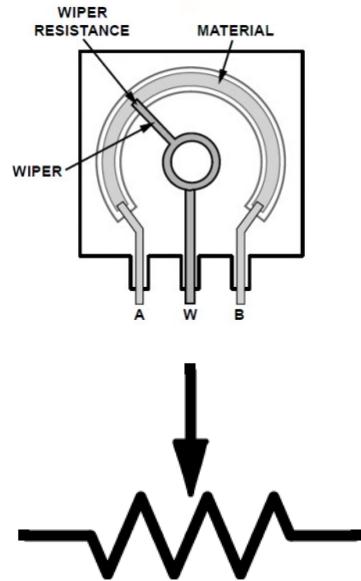


Light dependent
Resistor
(photoresistor)

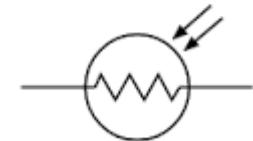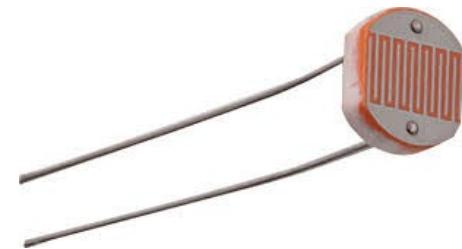


Switches

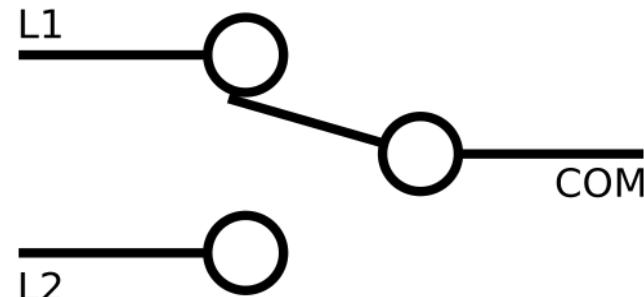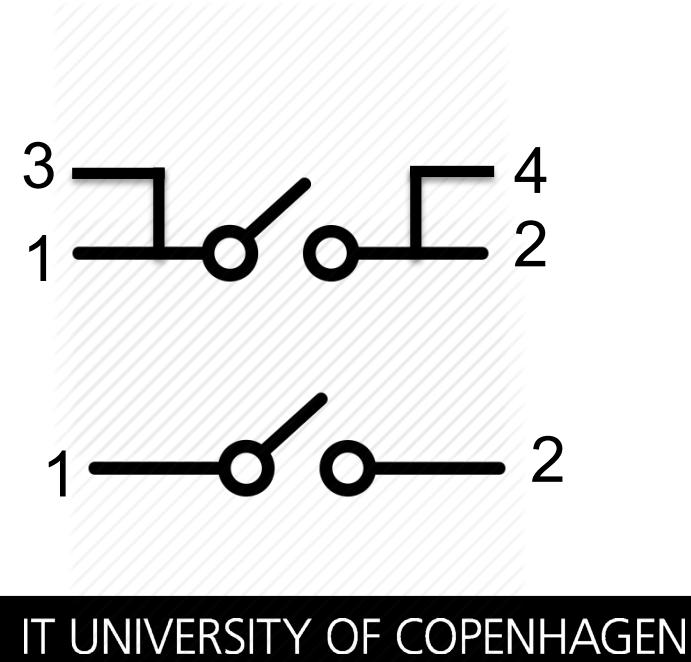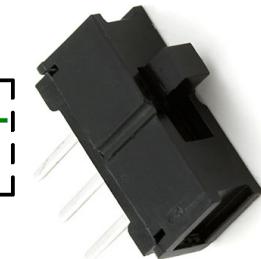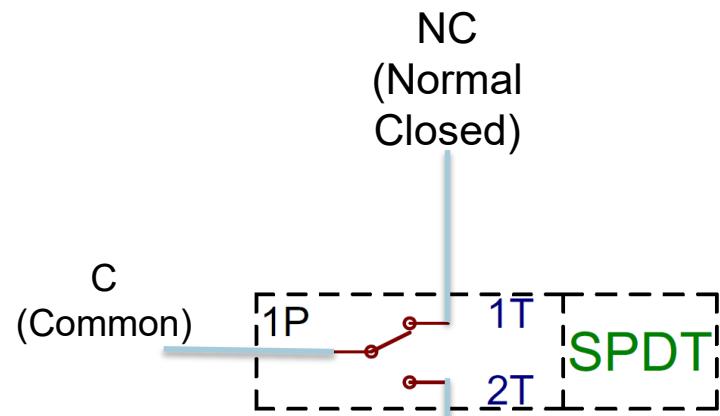

How to read a switch?

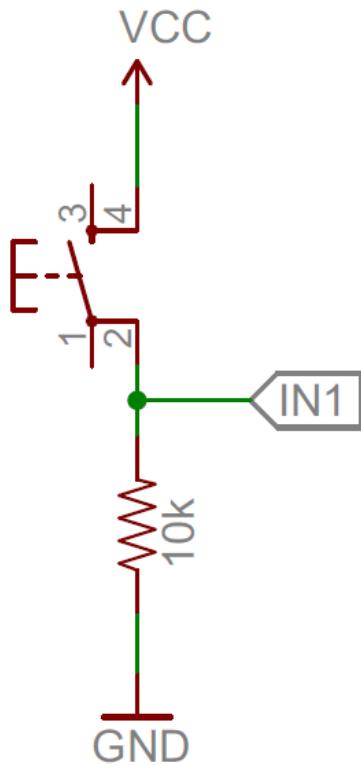


Positive Logic
(Pull-down)

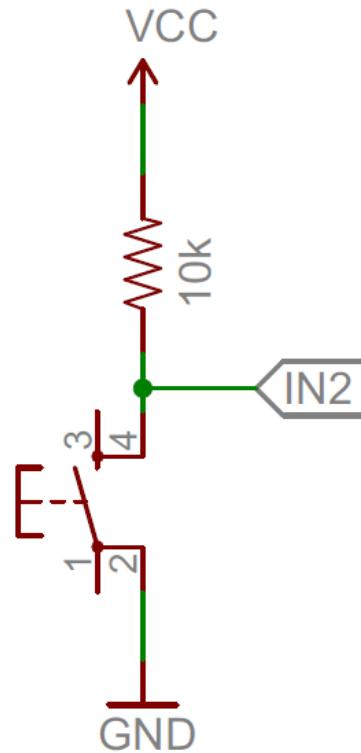


Negative Logic
(Pull-up)

Potentiometer

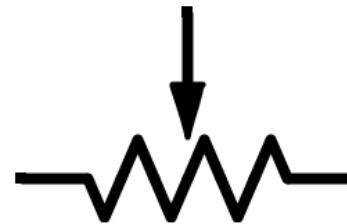


3 terminals
Polarity

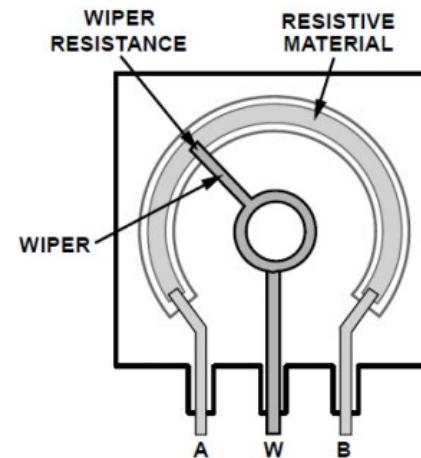


How to read a potentiometer?

potentiometer input

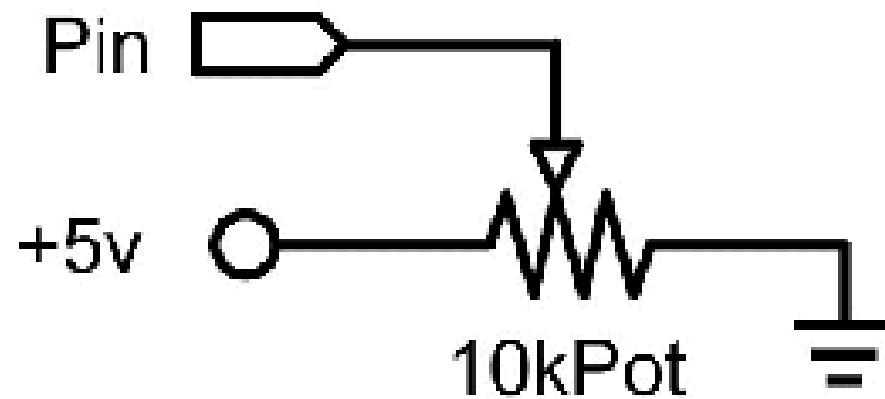

Light dependent Resistor (photoresistor)

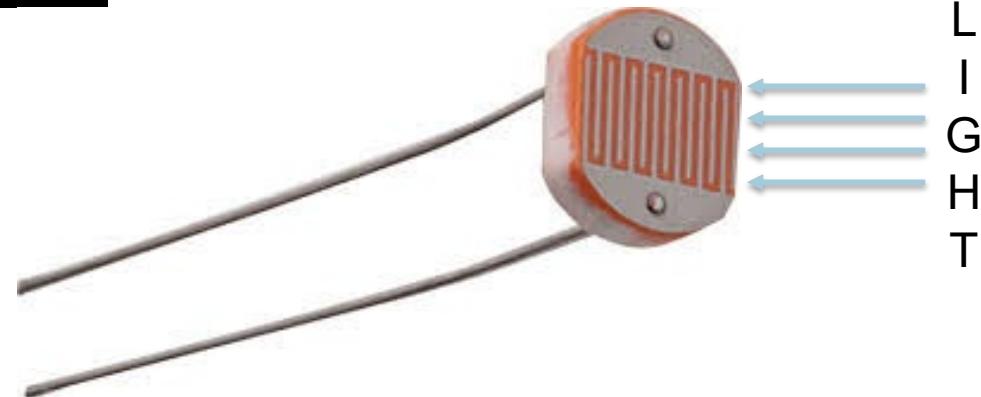


2 Terminals


No polarity

Like a resistor

Resistance changes with received light

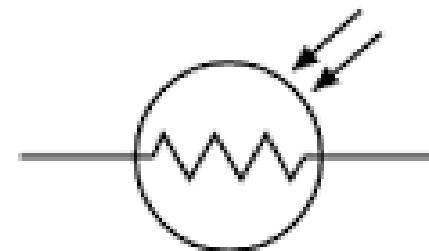


How to read a photoresistor?


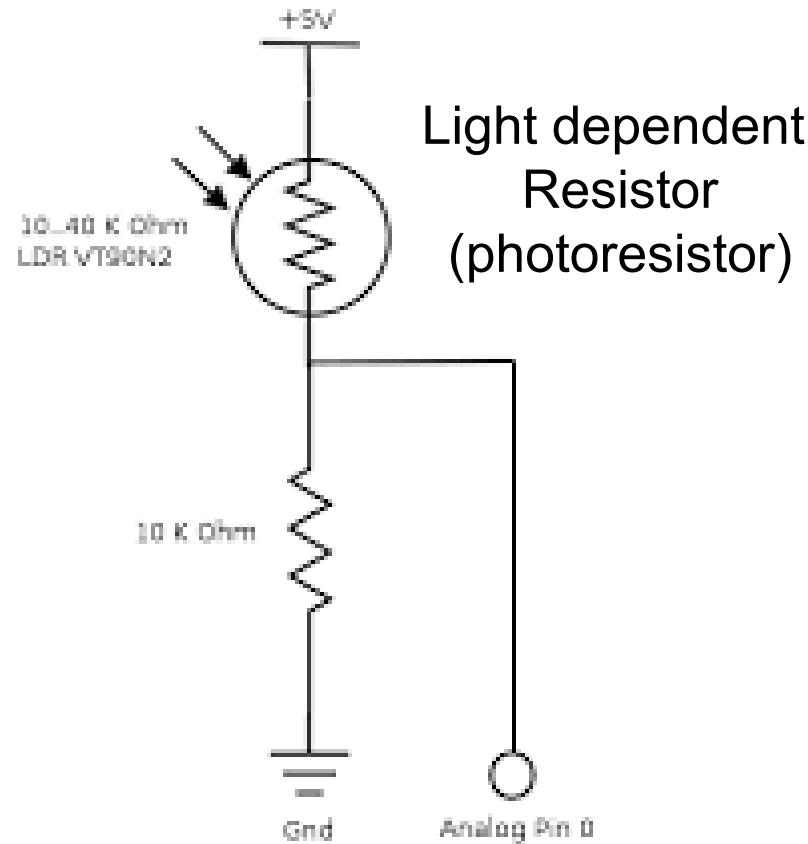


Optosensors

Reflective optosensors

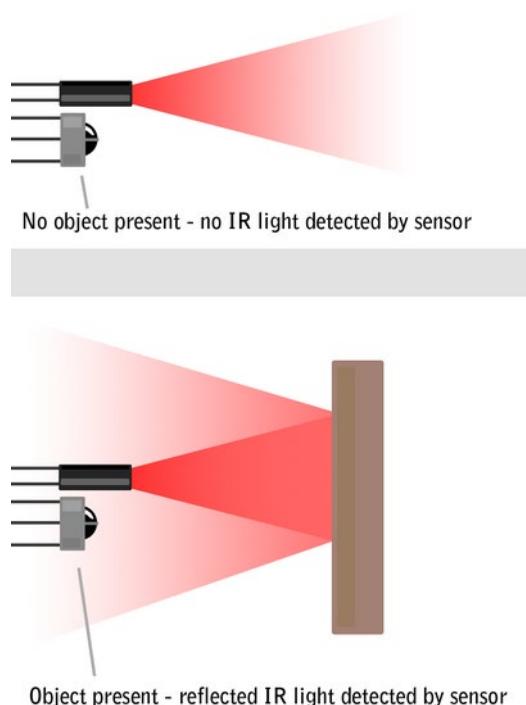



Break beam optosensors

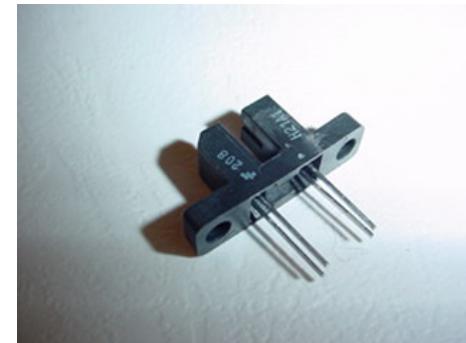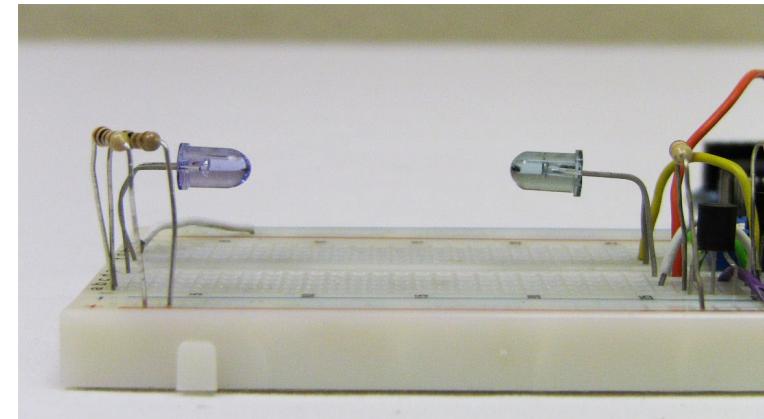

Light sensor tricks

- Polarized light
- Infrared light
- Modulation/demodulation

An IR sensor

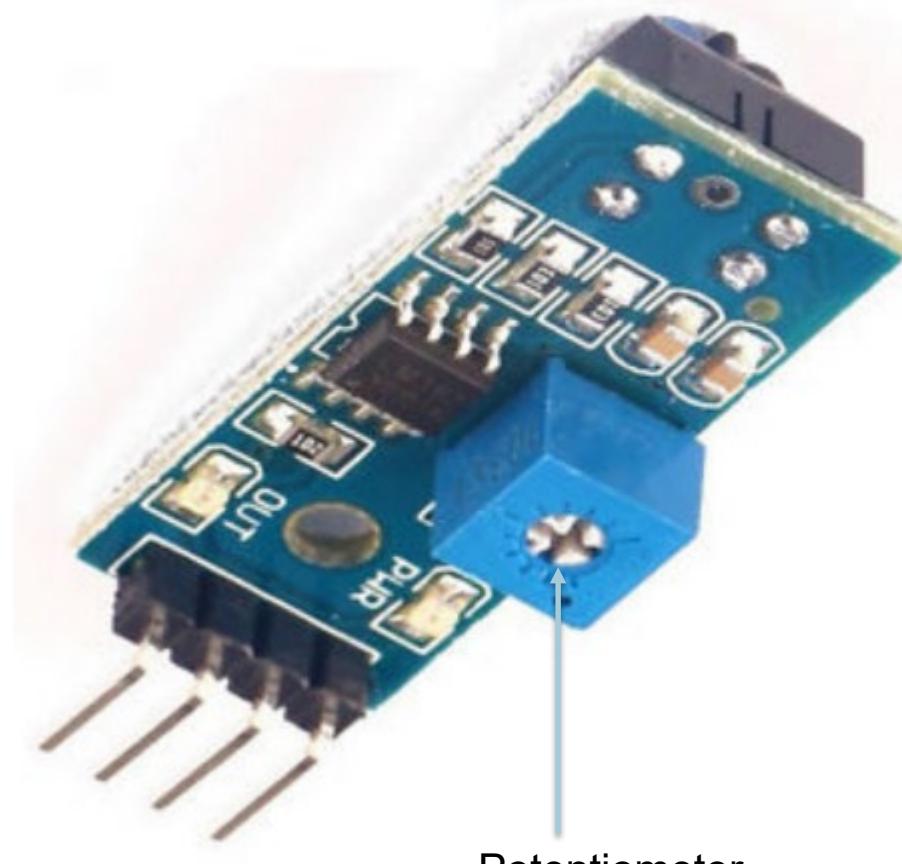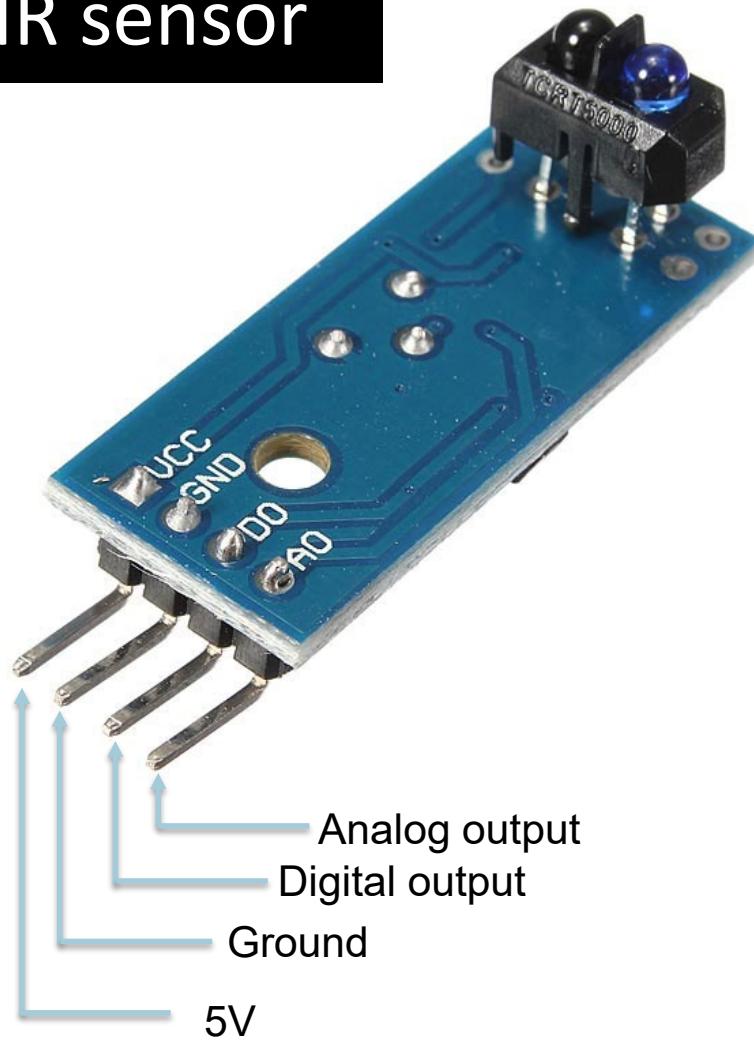


Potentiometer
(adjust the threshold
for the digital output)

Digital output: 0 or 5V, <10mA

Analog output: 0 – 5V, <10mA

Roomba

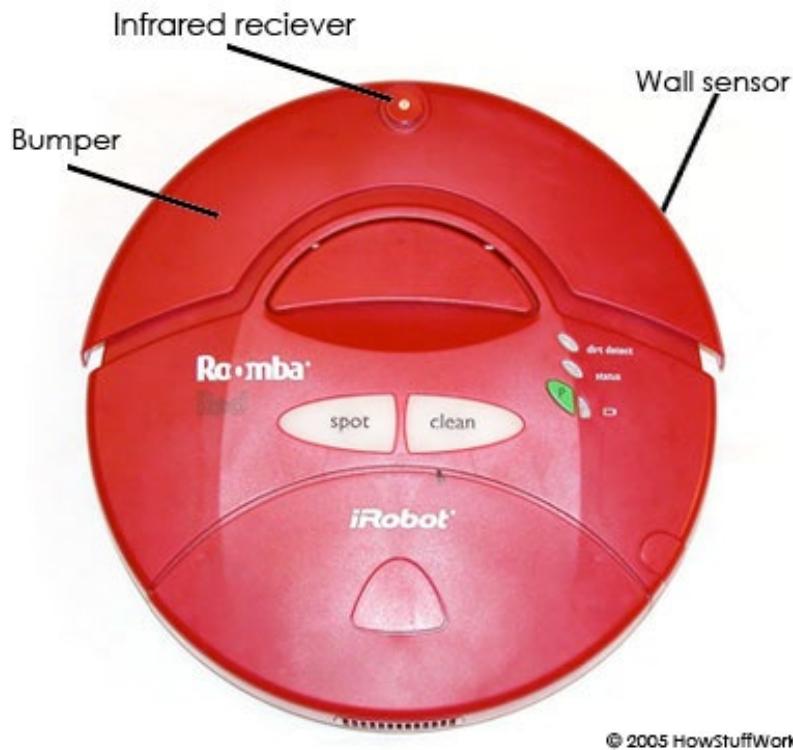


Reflective
optosensor

Switches


Cliff sensors

Object sensors

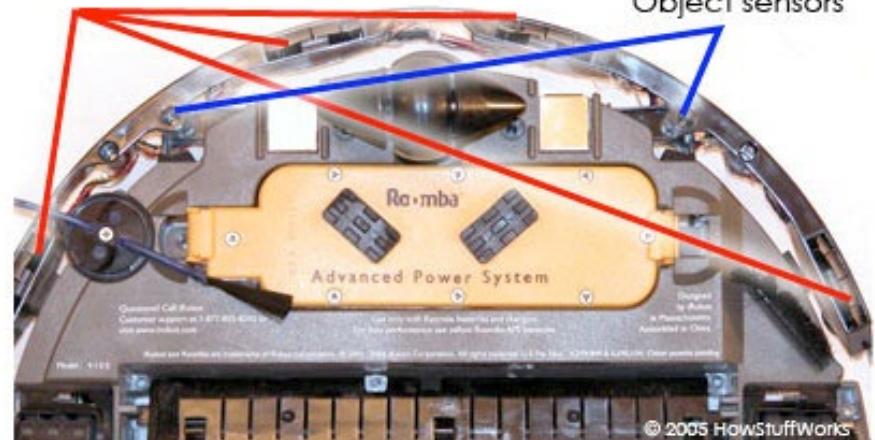


<http://electronics.howstuffworks.com/gadgets/home/robotic-vacuum2.htm>

Shaft encoders

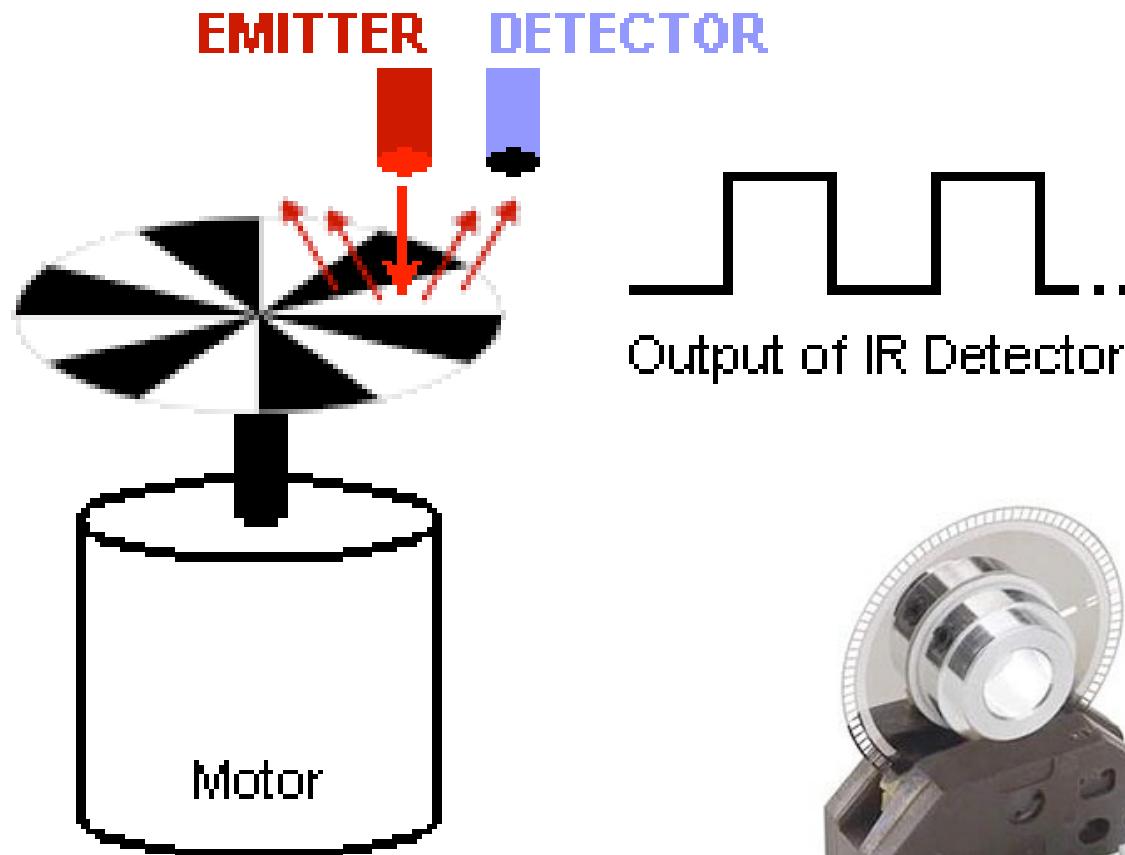


Robot arm joint uses shaft encoders

Relative position

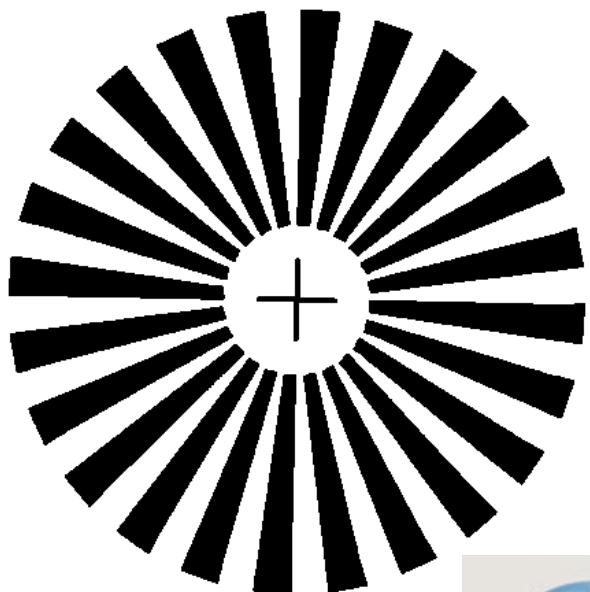

Absolut position

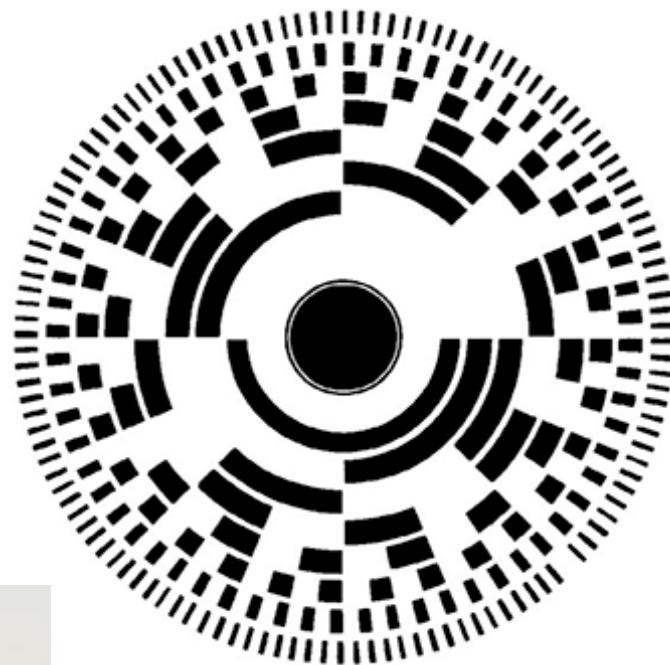

Bar codes also possible








Advanced sensors

- Ultra-sonic and sonar sensors (sound's time of flight)
- Laser sensing (pinpoint accuracy, light's time of flight)
- Visual sensing (array of light sensors, cameras)
- Microphones

Exercise #2 - Test simple sensors

Making things move

Basics concepts

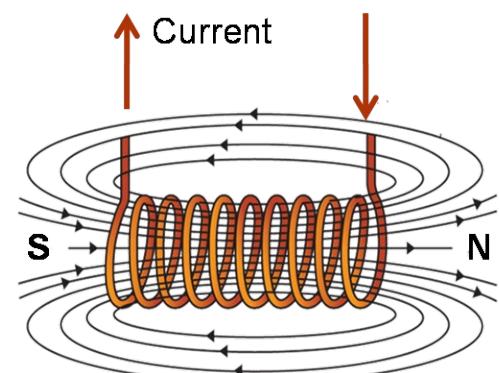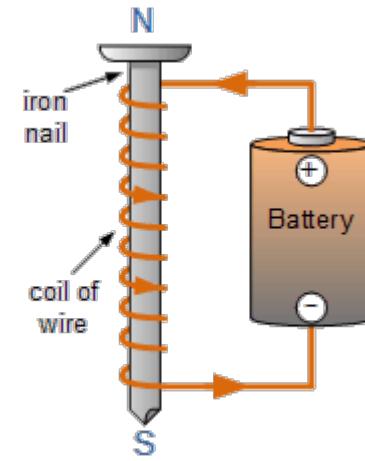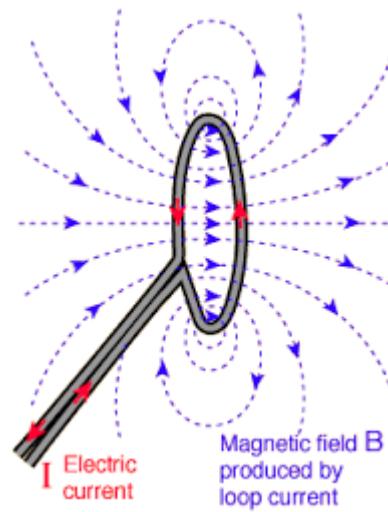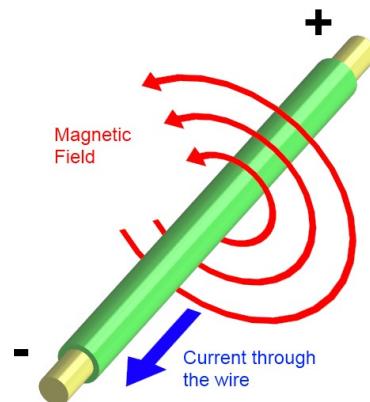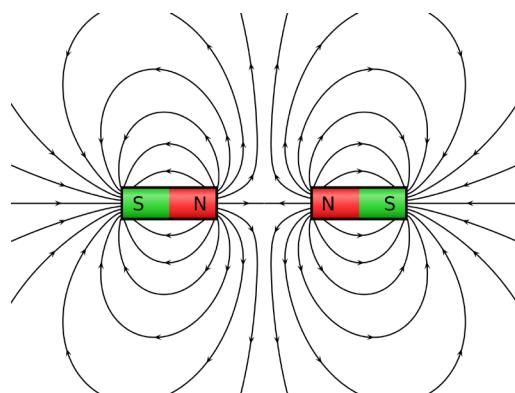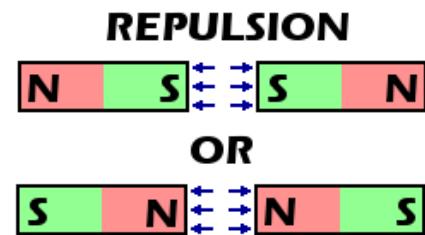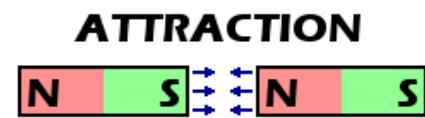


magnet.fsu.edu

DC - Motor



DC – Motor – The clever bit

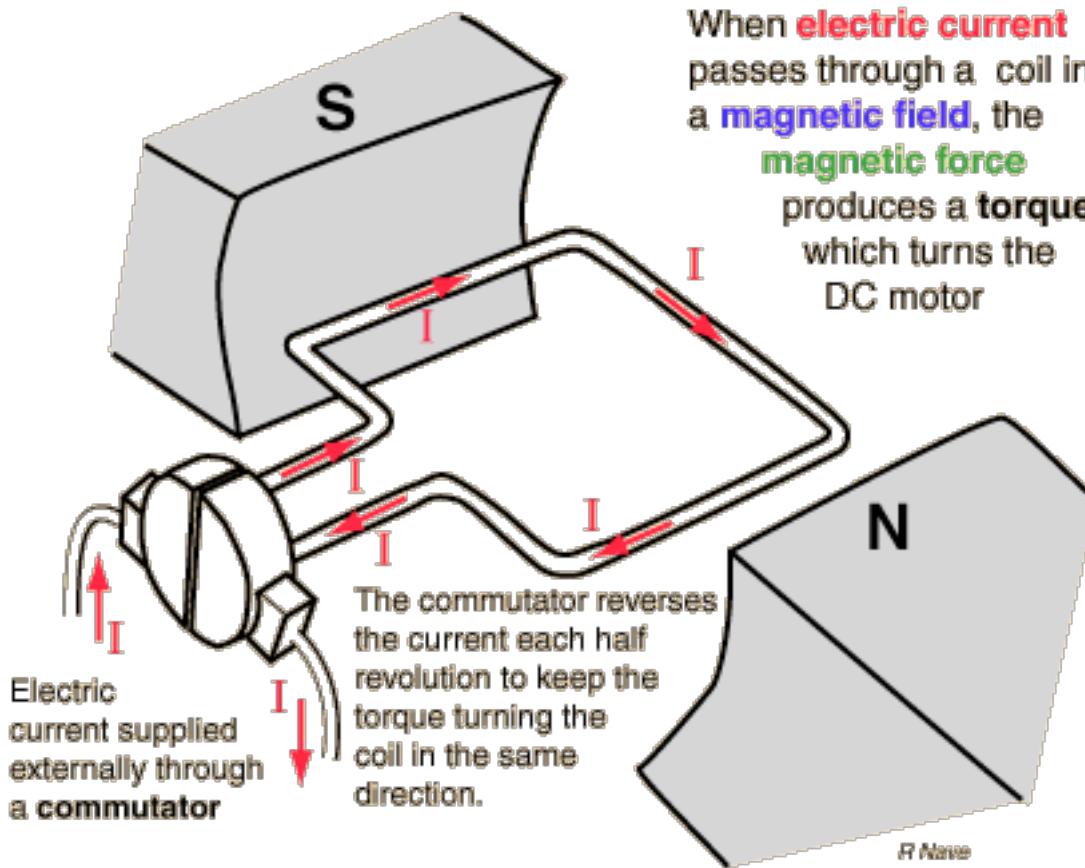


wiseGEEK

Brushed DC motor

Many variation of this design used

DC motor + reduction

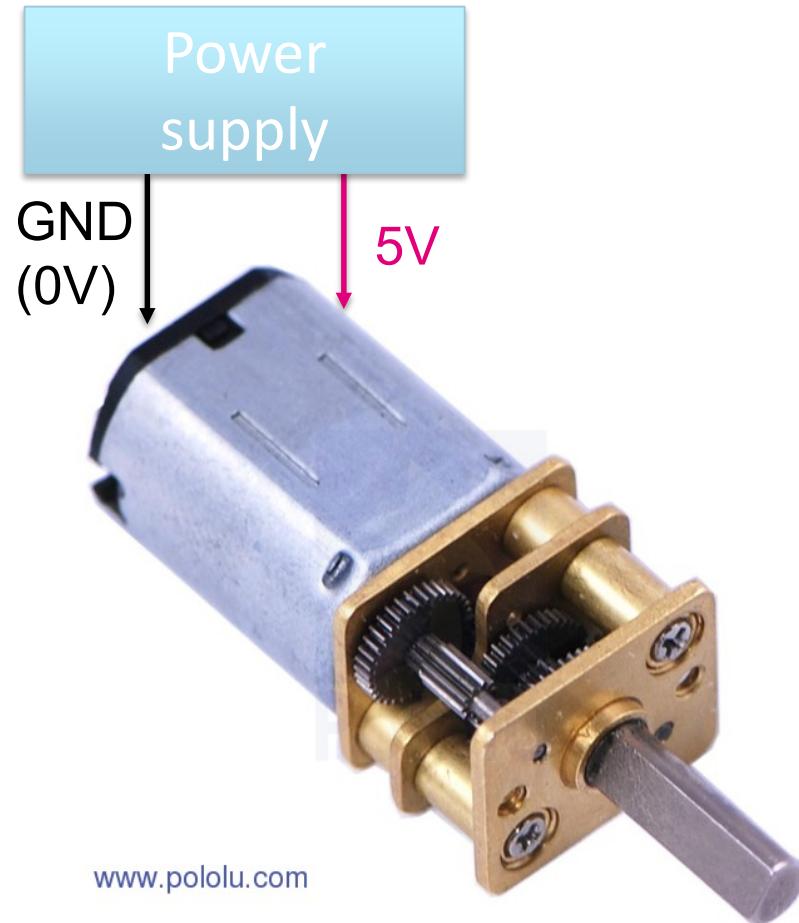

www.pololu.com

Motor Type	Stall Current @ 6 V	No-Load Speed @ 6 V	Approximate Stall Torque @ 6 V	Single-Shaft (Gearbox Only)
high-power, carbon brushes (HPCB)	1600 mA	3000 RPM	4 oz-in	10:1 HPCB
		1000 RPM	9 oz-in	30:1 HPCB
		625 RPM	15 oz-in	50:1 HPCB
		400 RPM	22 oz-in	75:1 HPCB
		320 RPM	30 oz-in	100:1 HPCB
		200 RPM	40 oz-in	150:1 HPCB
		140 RPM	50 oz-in	210:1 HPCB
		120 RPM	60 oz-in	250:1 HPCB
		100 RPM	70 oz-in	298:1 HPCB
		32 RPM	125 oz-in	1000:1 HPCB



Exercise #3 – Test a DC motor



Connect the dc motor to a power supply
Always use less than 6V!

What happens if
you change the polarity
you change the voltage (<6V)
break the shaft of the motor (**don't stop it**)

Check also what happens with the intensity




DC motor - Control

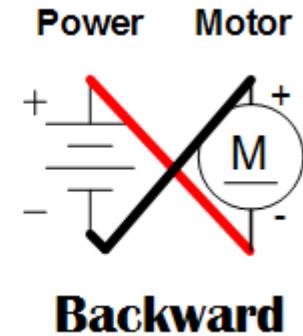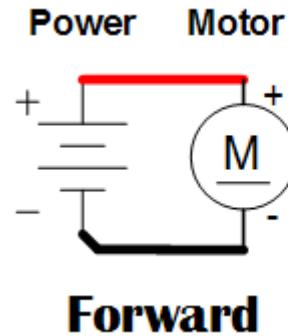- Constant voltage
- Change direction
 - Reverse polarity
- Speed proportional to the voltage
- Speed depends on the load
- Torque proportional to the I



A motor consumes a lot of current (>200mA)!

DC motor – H-bridge

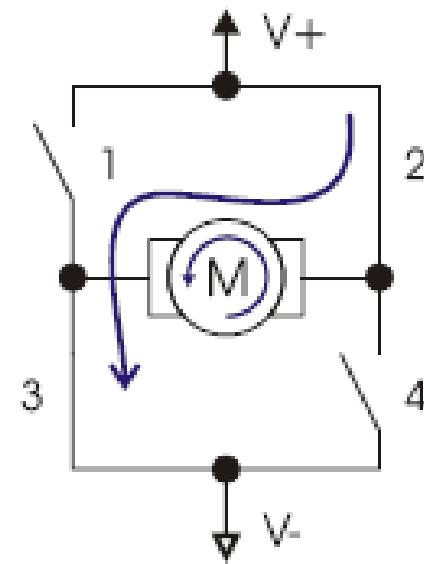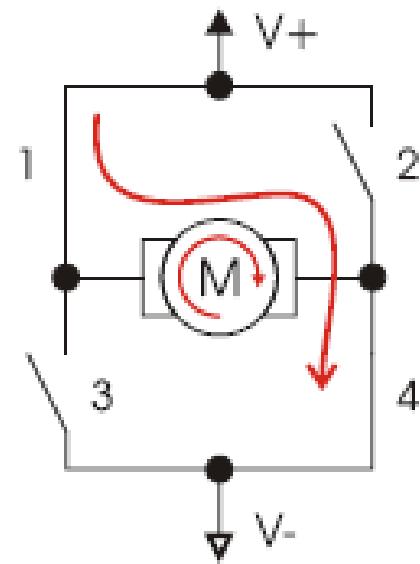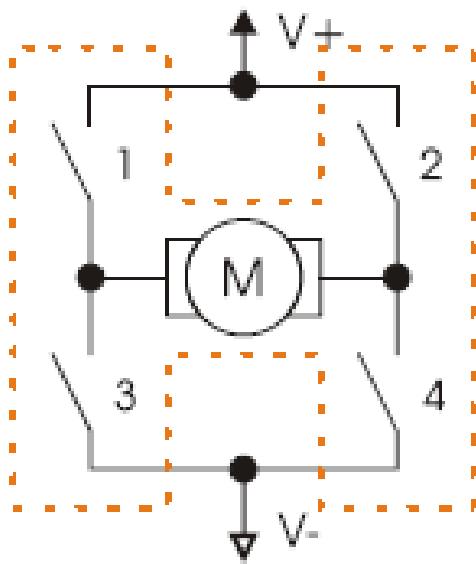


Problem

Our motor consumes high currents (>200mA)


Our IR sensors are only able to give 10mA

How can we control our robots?????

Diode

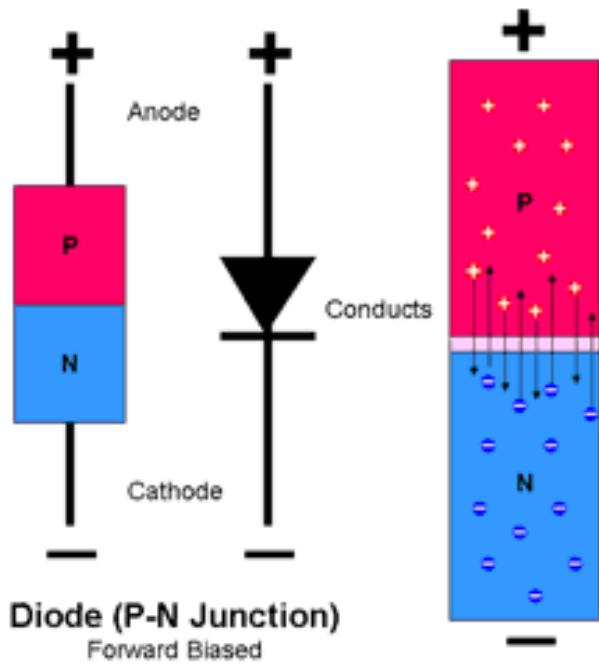

Forward biased diode

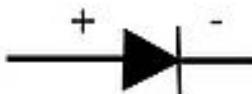


Electron flow ←

Current flow →



Reverse biased diode

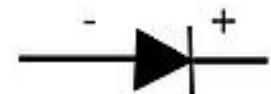


Electron flow - None

Current flow - None




A LED is a
diode that
emits light!

Transistor – npn


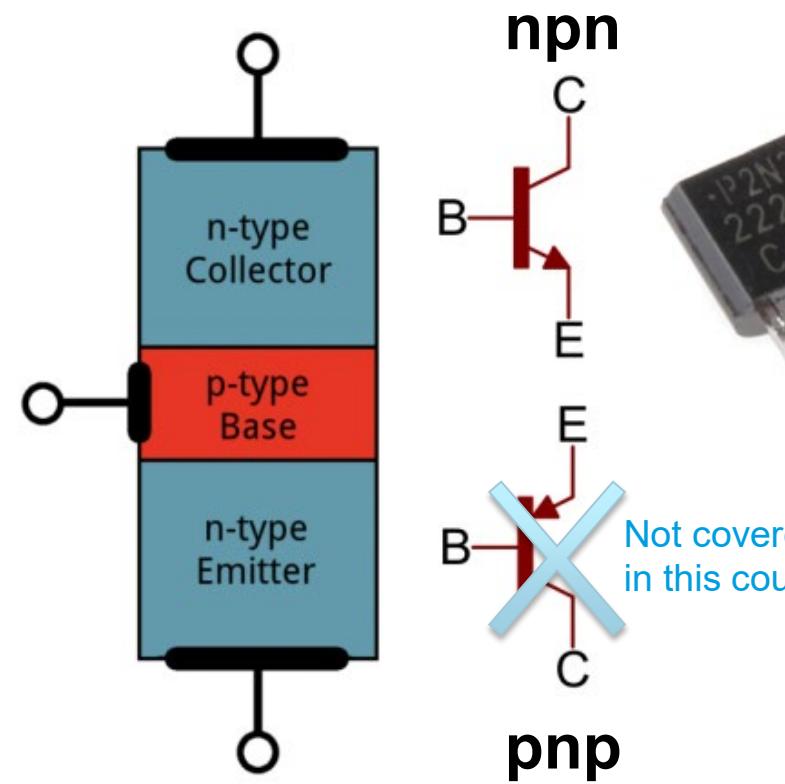


Not covered
in this course


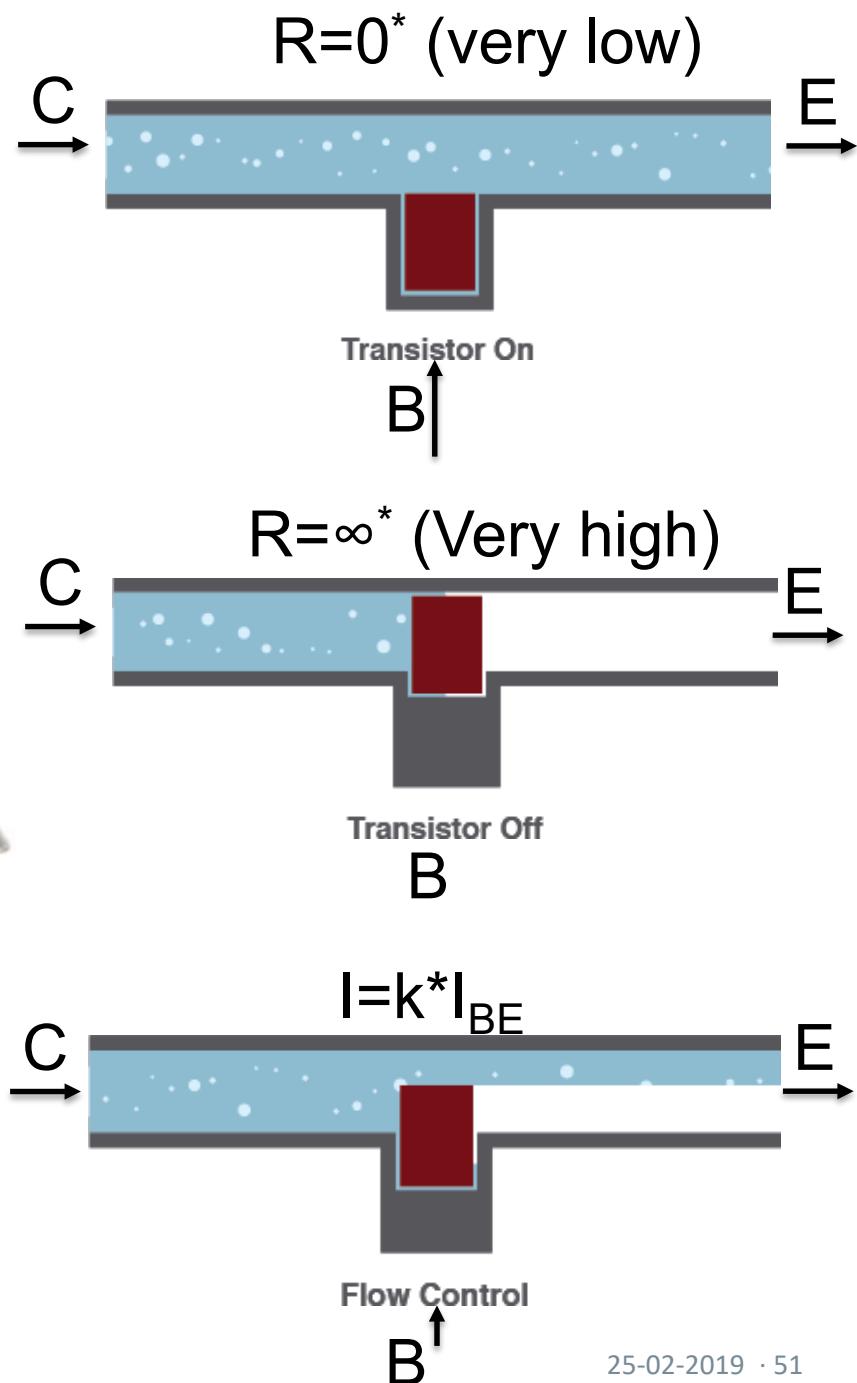


Some of them are able to handle high currents from collector to emitter!

Transistor – Circuit

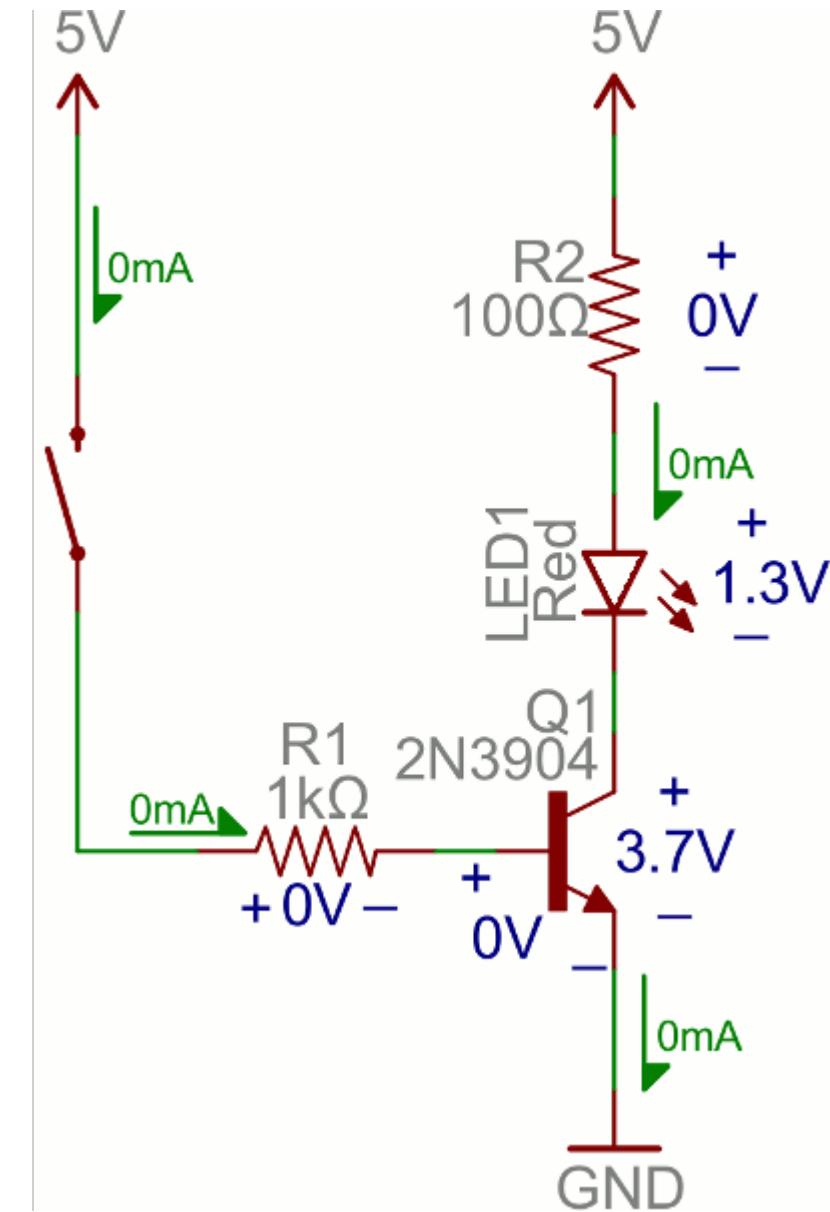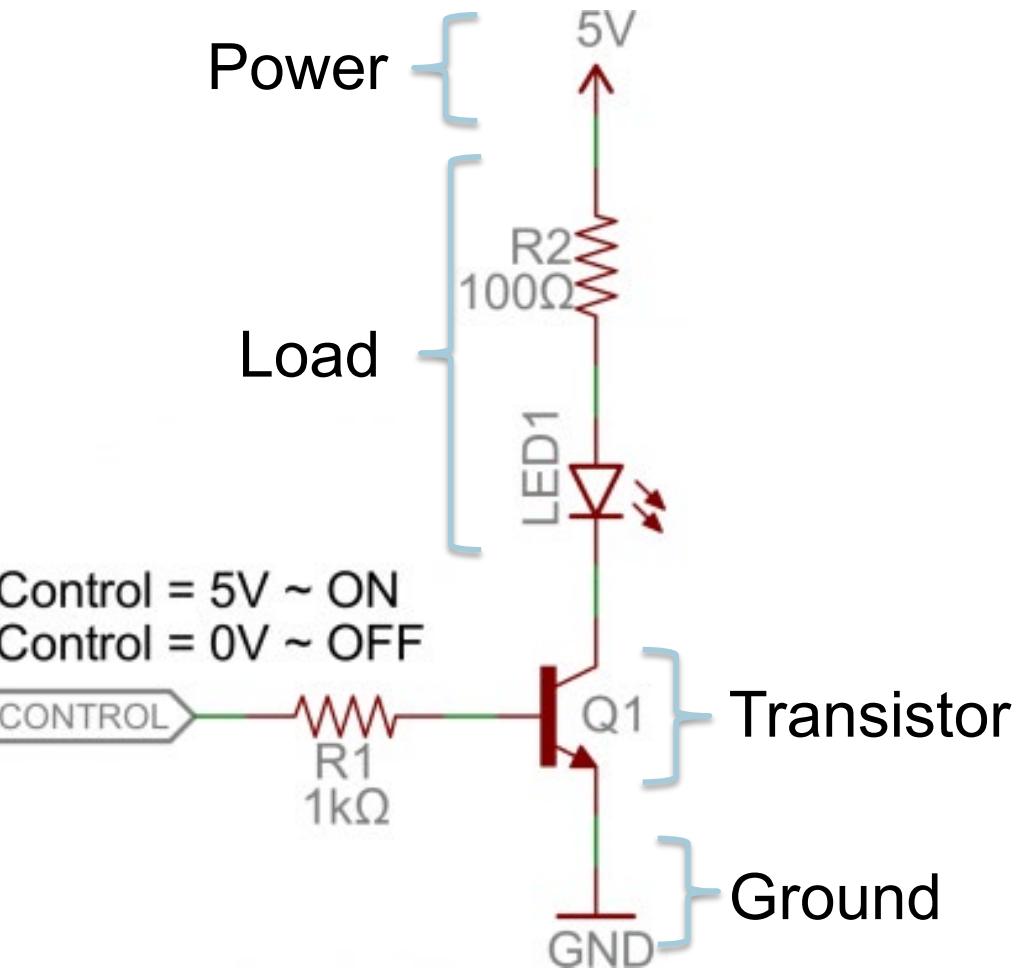



Transistor – Switch applications

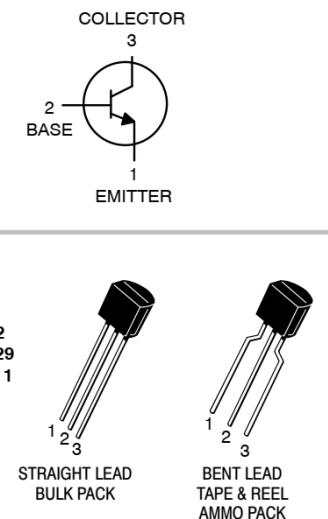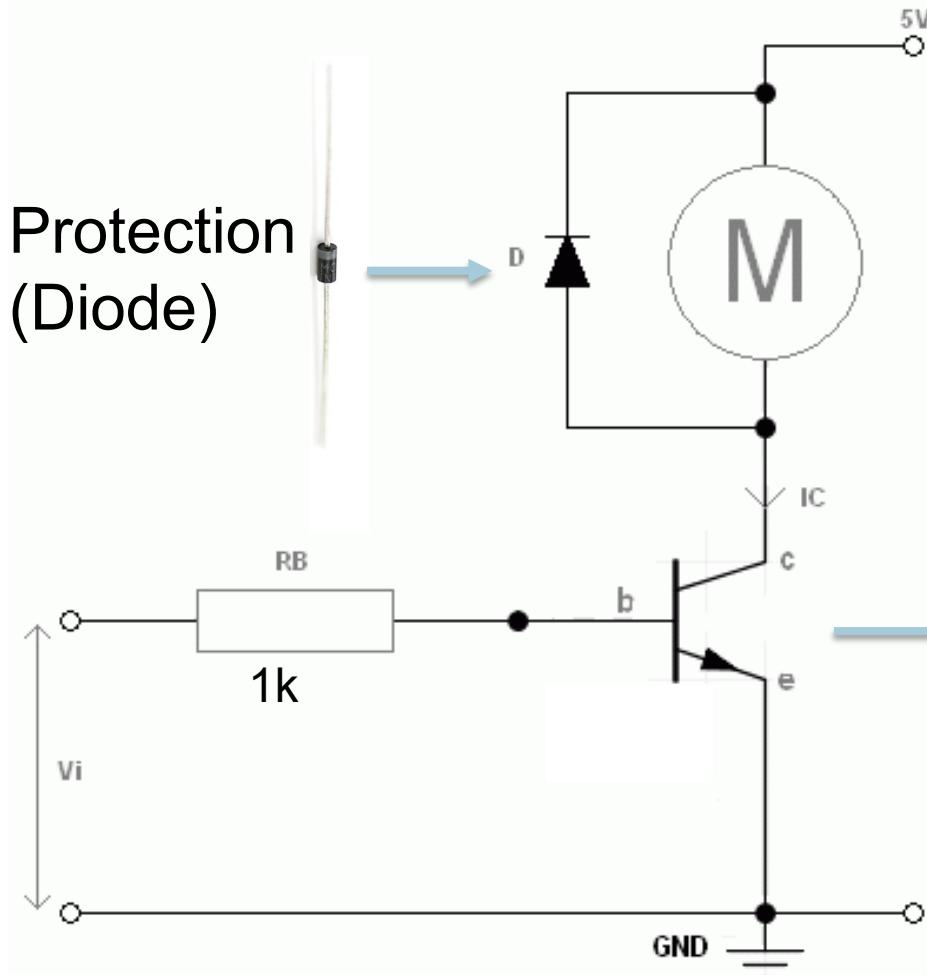


© www.petervis.com

DC motor - Control

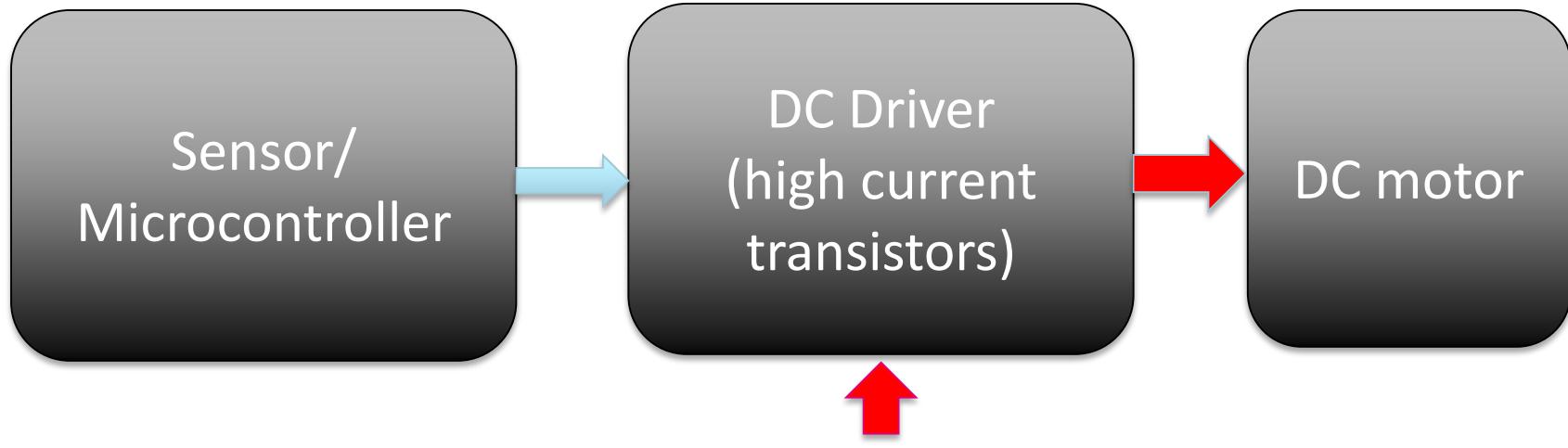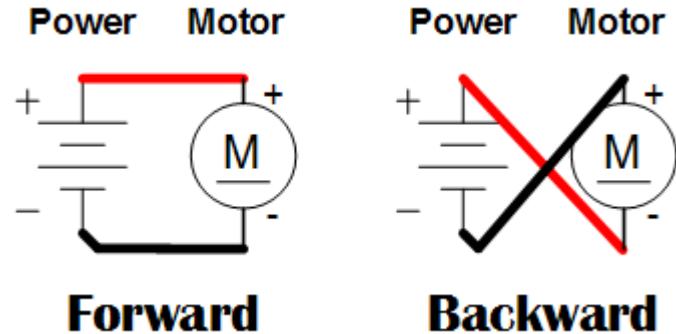
- Change direction
 - Reverse polarity
- Constant voltage
- Speed proportional to the voltage




Transistor - H-bridge

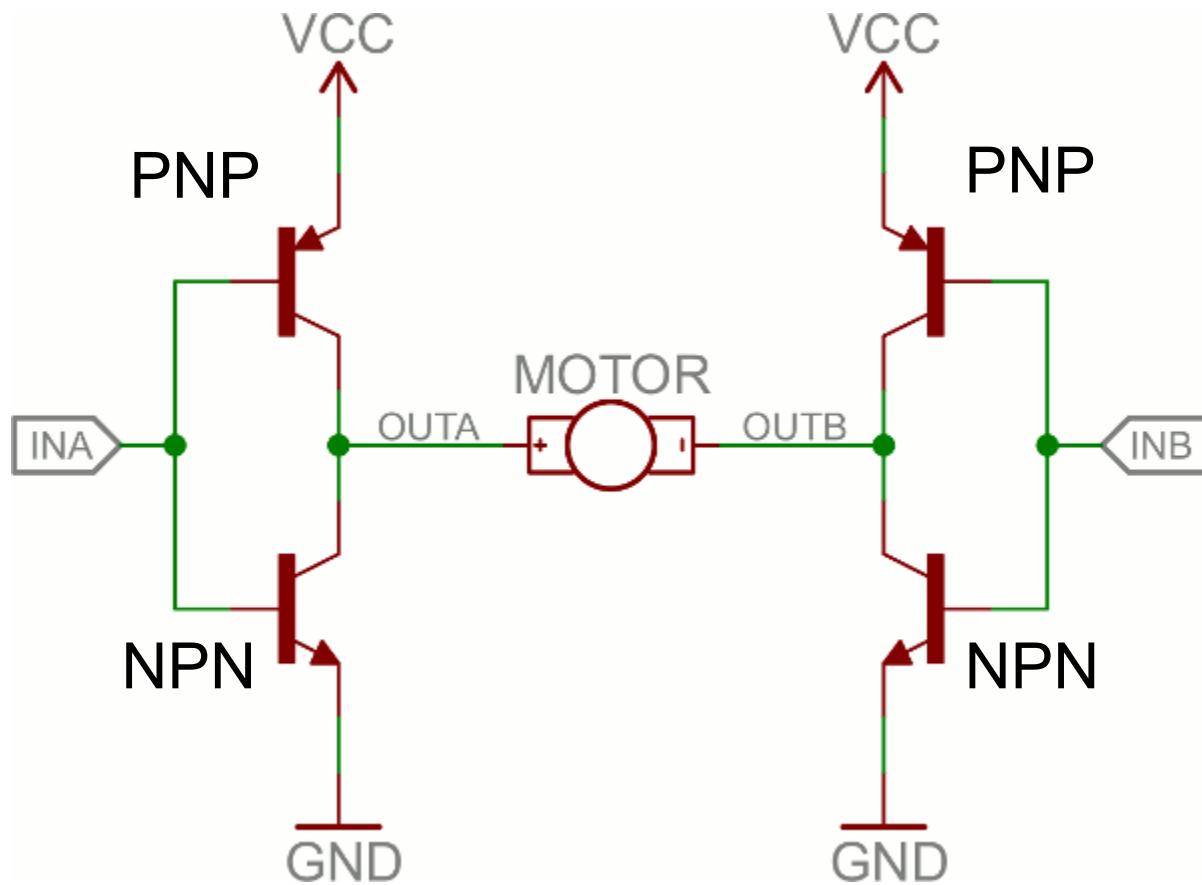


Transistor – Logic switches

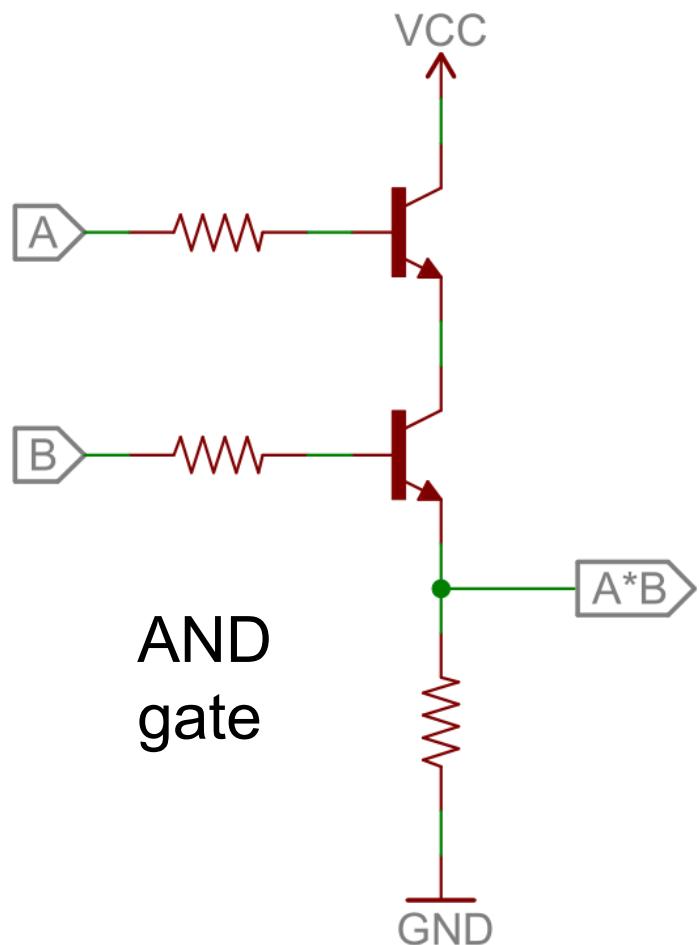

AND
gate

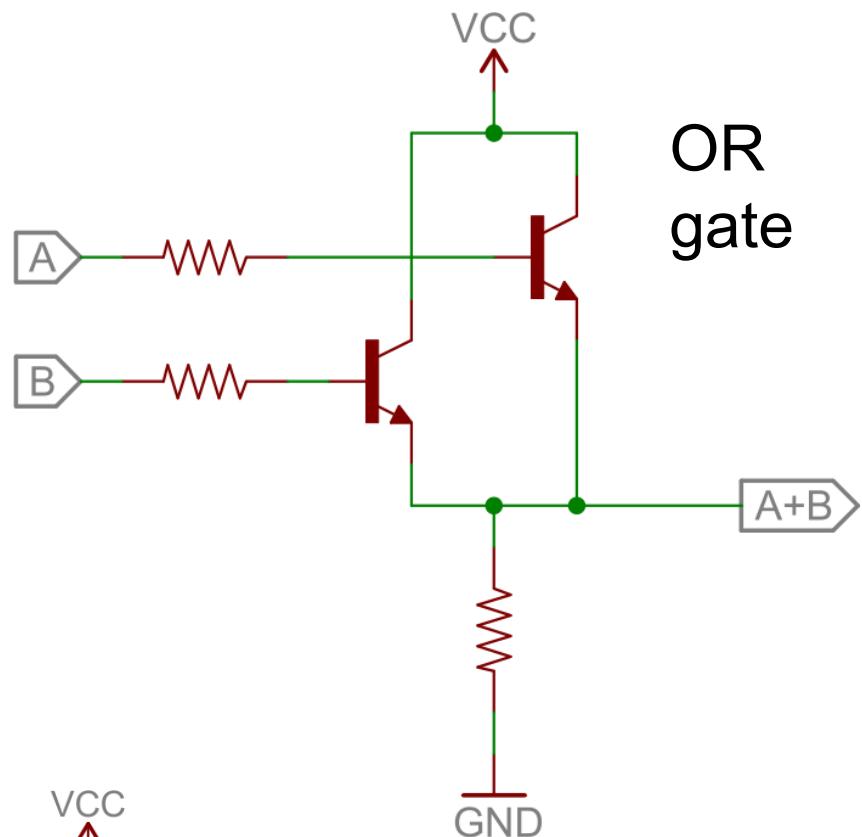

OR
gate

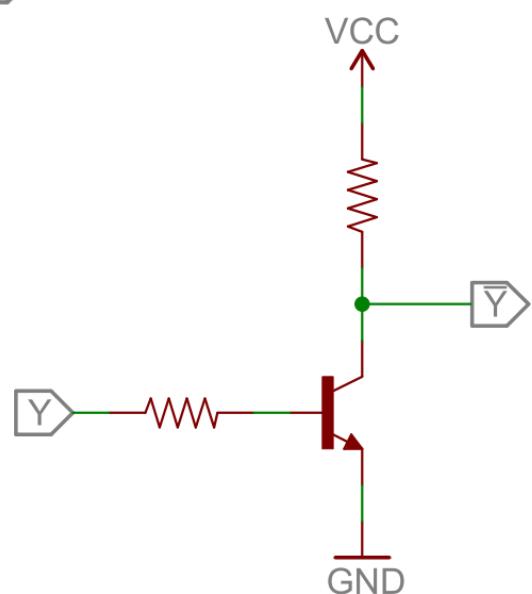

NOT
gate

Do we really need computers?



Tortoise - Grey Walters – 1948 - 1951

Mandatory assignment

Use **IR sensors** to make a robot that follows a line

Use **switches** to make a robot that avoids obstacles

Place the sensors on the robot

(double sided tape/hot glue?)

Use the digital or analog output of the sensors

Check how the output of the IR sensor changes

with different surfaces/objects

with different distance to object

with different lights

measure noise

Use two transistors to control the motors

If your robot uses stepper drivers:

Use a dc motor + sensors from the kit

Do not use your robot (we will use it in next lecture)

Danger!

Motors, electronic components (and students) can be damaged easily

Double check the wiring

Take care of different voltage levels

If you are not sure, ASK!

Where to find electric components?

Components:

Sensors

Shields

Breakout boards

Distributors:

RS Components (www.rs-components.com/)

Mouser (www.mouser.dk/)


TME (<https://www.tme.eu/en/>)

DIY shops (with tutorials and libraries):


Adafruit (<https://www.adafruit.com/>)

Sparkfun (<https://www.sparkfun.com/>)

Tips – Obstacle avoidance

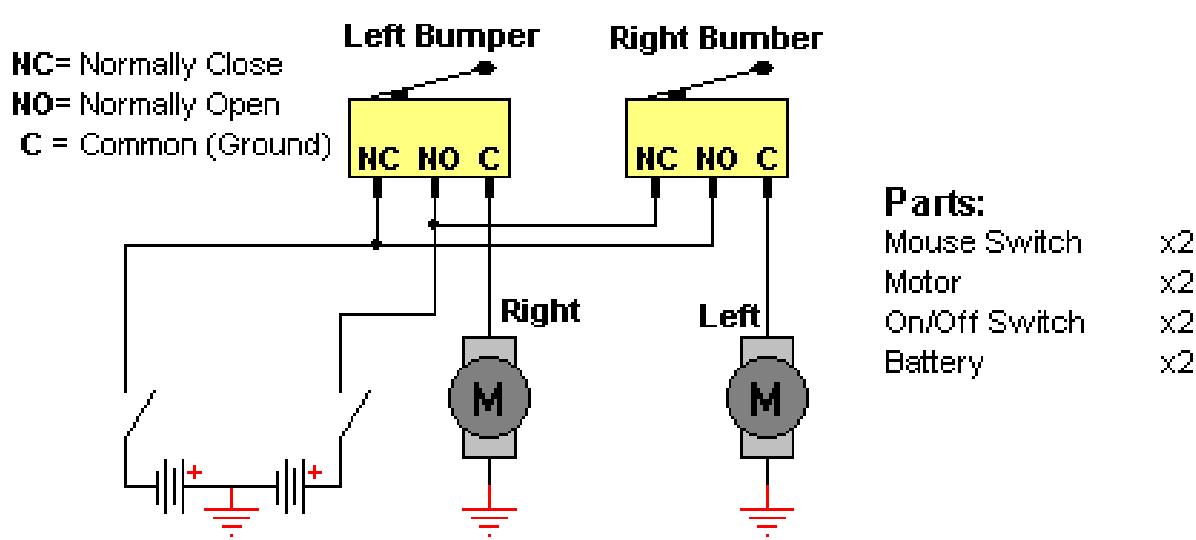

Tips – Line follower

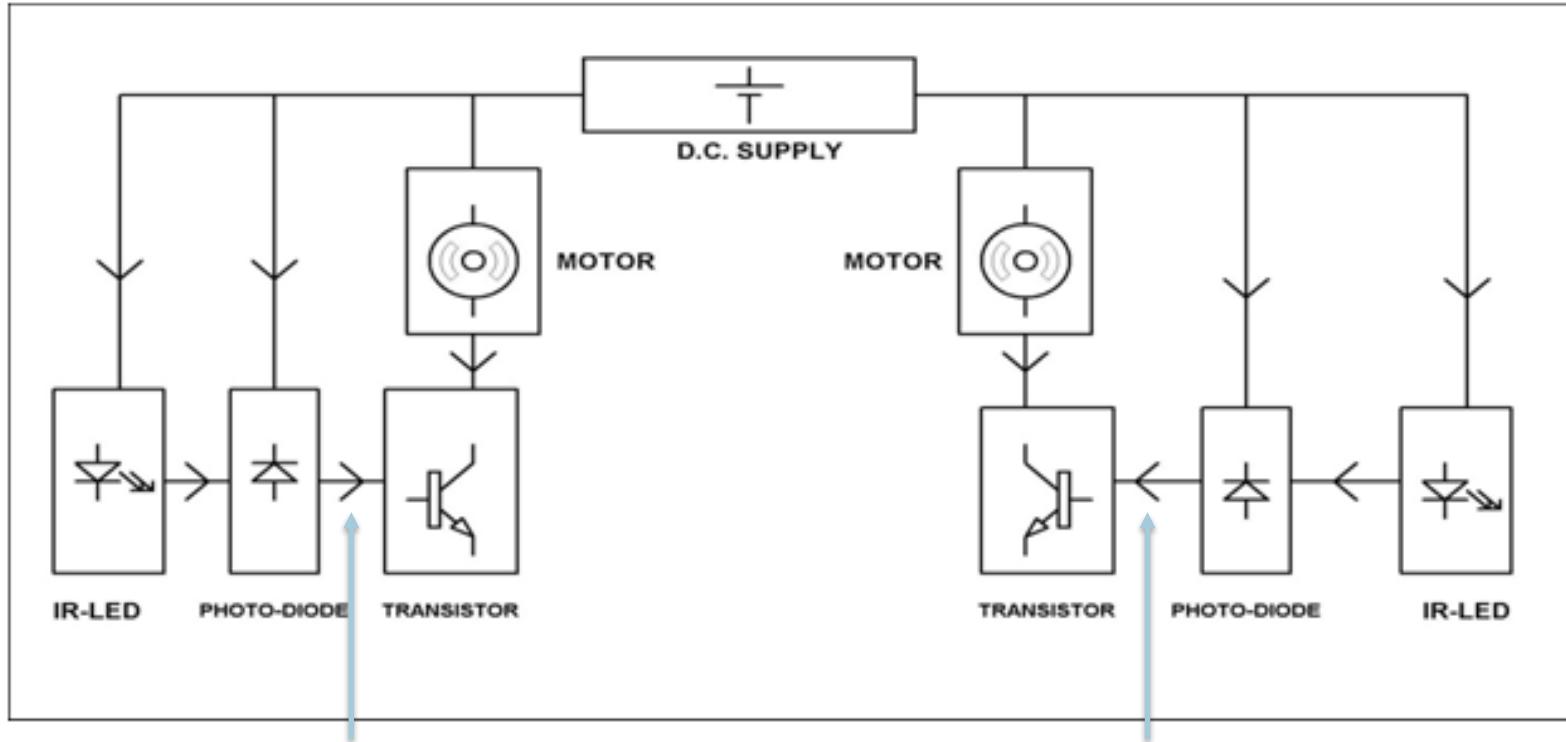

Remember the resistors on the base of the transistors
(470 ohm)




Transistors

Do not use the temp sensor (same shape)


We have two different kind of transistors:

PN2222, BC337

Check how to wire them

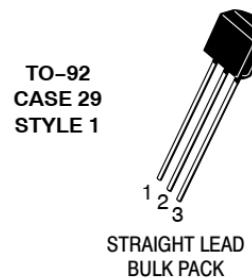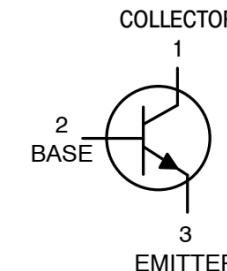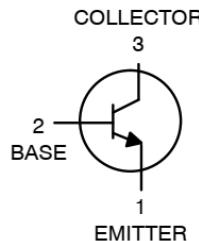

PN2222

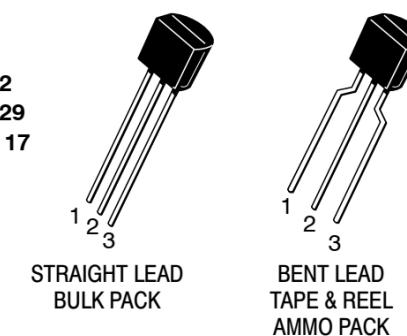

BC337

Ready?

Let's connect some wires!

Andrés Faíña, 4D26
anfv@itu.dk